

# Digital logic: Gates, Truth tables, logic equations

Yipeng Huang

Rutgers University

April 20, 2021

# Table of contents

Announcements

Transistors: The building block of computers

Combinational logic

- Basic gates

- More-than-2-input gates

# Looking ahead

## Class plan

1. PA5 due Monday, 4/26.
2. Digital logic. Reading assignment: CS:APP Chapter 4.2. Recommended reading: Patterson & Hennessy, Computer organization and design, appendix on "The Basics of Logic Design." Available online via Rutgers Libraries.

# Table of contents

Announcements

Transistors: The building block of computers

Combinational logic

- Basic gates

- More-than-2-input gates

# Computer organization


## Layer cake

- ▶ Society
- ▶ Human beings
- ▶ Applications
- ▶ Algorithms
- ▶ High-level programming languages      **Java, Python**
- ▶ Interpreters
- ▶ Low-level programming languages      **C, assembly**
- ▶ Compilers
- ▶ Architectures
- ▶ Microarchitectures
- ▶ Sequential/combinational logic
- ▶ Transistors
- ▶ Semiconductors
- ▶ Materials science
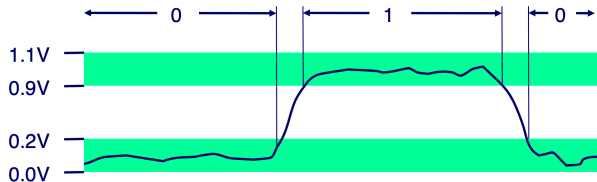
## Everything is bits

Data representation: bits, ints, floats

- Each bit is 0 or 1
- By encoding/interpreting sets of bits in various ways
  - Computers determine what to do (instructions)
  - ... and represent and manipulate numbers, sets, strings, etc...
- Why bits? Electronic Implementation
  - Easy to store with bistable elements
  - Reliably transmitted on noisy and inaccurate wires



# To build logic, we need switches

## Vacuum tubes a.k.a. valves



**Figure:** Source: By Stefan Riepl (Quark48) - Self-photographed, CC BY-SA 2.0

<https://commons.wikimedia.org/w/index.php?curid=14682022>

## Transistors



**Figure:** Source: Wikimedia

- ▶ The first transistor developed at Bell Labs, Murray Hill, New Jersey
- ▶ <https://www.bell-labs.com/about/locations/murray-hill-new-jersey-usa/>

# MOSFETs

## MOS: Metal-oxide-semiconductor

- ▶ A sandwich of conductor-insulator-semiconductor.

## FET: Field-effect transistor

- ▶ Gate exerts electric field that changes conductivity of semiconductor.



# NMOS, PMOS, CMOS

## PMOS: P-type MOS

- ▶ positive gate voltage, acts as open circuit (insulator)
- ▶ negative gate voltage, acts as short circuit (conductor)

## NMOS: N-type MOS

- ▶ positive gate voltage, acts as short circuit (conductor)
- ▶ negative gate voltage, acts as open circuit (insulator)

## CMOS: Complementary MOS

- ▶ A combination of NMOS and PMOS to build logical gates such as NOT, AND, OR.
- ▶ We'll go to slides posted in supplementary material to see how they work.

# Combinational vs. sequential logic

## Combinational logic

- ▶ No internal state nor memory
- ▶ Output depends entirely on input
- ▶ Examples: NOT, AND, NAND, OR, NOR, XOR, XNOR gates, decoders, multiplexers.

## Sequential logic

- ▶ Has internal state (memory)
- ▶ Output depends on the inputs and also internal state
- ▶ Examples: latches, flip-flops, Mealy and Moore machines, registers, pipelines, SRAMs.

# Table of contents

Announcements

Transistors: The building block of computers

Combinational logic


- Basic gates

- More-than-2-input gates

- All truth tables can be expressed in just NOT, AND and OR gates (sum-of-products form)

- Just either the NAND or the NOR gate are universal to implement all combinational logic


# NOT gate

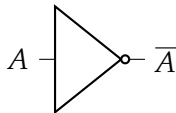

$A$	$\bar{A}$
0	1
1	0

**Table:** Truth table for NOT gate


# AND gate, NAND gate

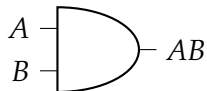

We write AND like a product

A	B	$AB$
0	0	0
0	1	0
1	0	0
1	1	1


Table: Truth table for AND gate

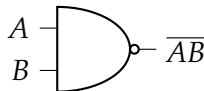

A	B	$\overline{AB}$
0	0	1
0	1	1
1	0	1
1	1	0

Table: Truth table for NAND gate


# OR gate, NOR gate

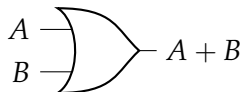

We write OR like a sum

$A$	$B$	$A + B$
0	0	0
0	1	1
1	0	1
1	1	1


Table: Truth table for OR gate

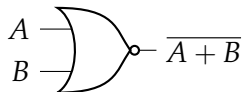

$A$	$B$	$\overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0


Table: Truth table for NOR gate

## XOR gate, XNOR gate

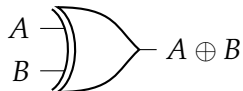

$A$	$B$	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0



Table: Truth table for XOR gate

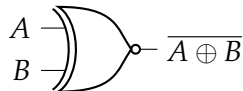

$A$	$B$	$\overline{A \oplus B}$
0	0	1
0	1	0
1	0	0
1	1	1

Table: Truth table for XNOR gate

## More-than-2-input AND gate

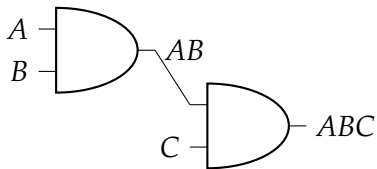
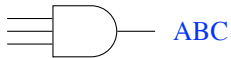


$A$	$B$	$C$	$ABC$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Table: Truth table for three-input AND gate



## More-than-2-input OR gate

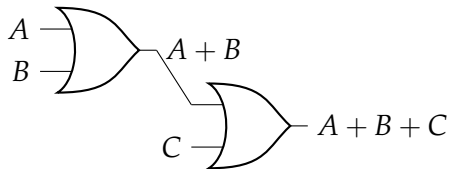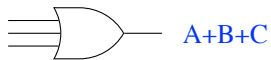

$A$	$B$	$C$	$A + B + C$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Table: Truth table for three-input AND gate