

Digital logic: Functional completeness, logic simplification

Yipeng Huang

Rutgers University

April 22, 2021

Table of contents

Announcements

Combinational logic

Definitions for more-than-2-input gates

Functional completeness

The set of logic gates {NOT, AND, OR} is universal

The NAND gate is universal

The NOR gate is universal

Basic algorithms for logic simplification

Looking ahead

Class plan

1. PA5 due Monday, 4/26.

Table of contents

Announcements

Combinational logic

Definitions for more-than-2-input gates

Functional completeness

The set of logic gates {NOT, AND, OR} is universal

The NAND gate is universal

The NOR gate is universal

Basic algorithms for logic simplification

Combinational vs. sequential logic


Combinational logic

- ▶ No internal state nor memory
- ▶ Output depends entirely on input
- ▶ Examples: NOT, AND, NAND, OR, NOR, XOR, XNOR gates, decoders, multiplexers.

Sequential logic

- ▶ Has internal state (memory)
- ▶ Output depends on the inputs and also internal state
- ▶ Examples: latches, flip-flops, Mealy and Moore machines, registers, pipelines, SRAMs.



More-than-2-input AND gate

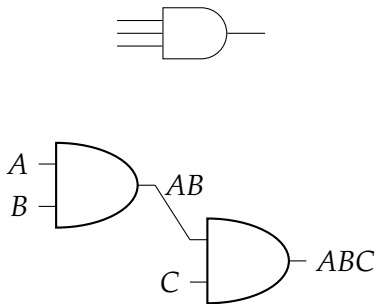

A	B	C	ABC
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Table: Truth table for three-input AND gate

More-than-2-input OR gate

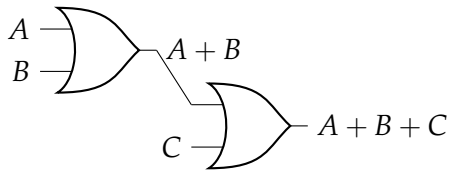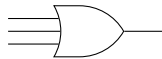

A	B	C	$A + B + C$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Table: Truth table for three-input AND gate

Table of contents

Announcements

Combinational logic

Definitions for more-than-2-input gates

Functional completeness

The set of logic gates {NOT, AND, OR} is universal

The NAND gate is universal

The NOR gate is universal

Basic algorithms for logic simplification

The set of logic gates {NOT, AND, OR} is universal

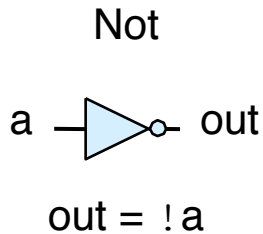
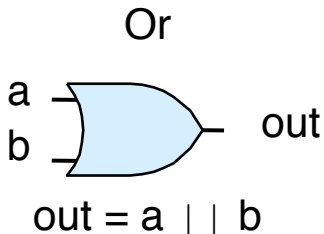
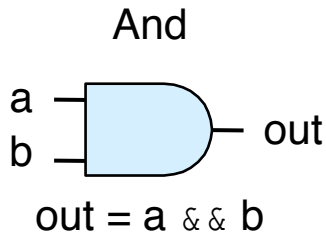


Figure: Source: CS:APP

The set of logic gates {NOT, AND, OR} is universal

- ▶ Any truth table can be expressed as sum of products form. Or'ing logical clauses consisting of and's

- ▶ Write each row with output 1 as a product (minterm).

- ▶ Sum the products (minterm).

- ▶ Forms a disjunctive normal form (DNF).

- ▶ $D = \bar{A}\bar{B}\bar{C} + A\bar{B}C$

- ▶ Always only needs NOT, AND, OR gates.


- ▶ Supplementary slides example...

Logical Completeness

Can implement ANY truth table with AND, OR, NOT.

A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

Sum of products
OR of AND clauses

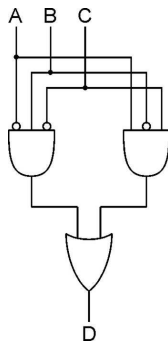


1. AND combinations that yield a "1" in the truth table.

2. OR the results of the AND gates.

The NAND gate is universal


NOT gate as a single NAND gate

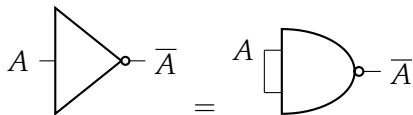

A	\bar{A}	AA	\overline{AA}
0	1	0	1
1	0	1	0

Table: $\bar{A} = \overline{AA}$

AND gate as two NAND gates

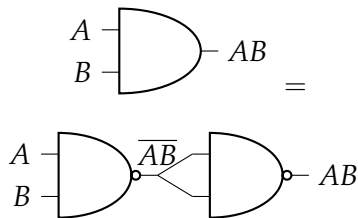

A	B	AB	\overline{AB}	$\overline{\overline{AB}}$
0	0	0	1	0
0	1	0	1	0
1	0	0	1	0
1	1	1	0	1

Table: $AB = \overline{\overline{AB}}$



The NAND gate is universal

De Morgan's Law

A	B	\bar{A}	\bar{B}	$\bar{A}\bar{B}$	$A + B$	$\overline{\bar{A}\bar{B}}$
0	0	1	1	1	0	1
0	1	1	0	0	1	0
1	0	0	1	0	1	0
1	1	0	0	0	1	0


Table: $\bar{A}\bar{B} = \overline{A + B}$

OR gate as three NAND gates

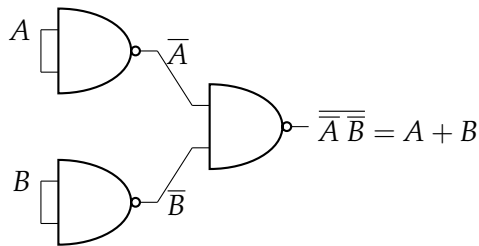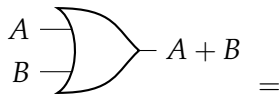

The NOR gate is universal


NOT gate as a single NOR gate

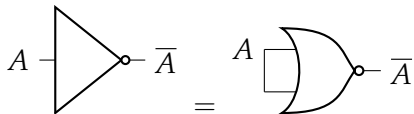

A	\bar{A}	$A + A$	$\overline{A + A}$
0	1	0	1
1	0	1	0

Table: $\bar{A} = \overline{A + A}$

OR gate as two NOR gates

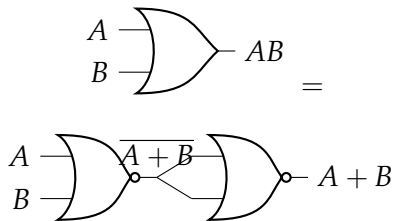

A	B	$A + B$	$\overline{A + B}$	$\overline{\overline{A + B}}$
0	0	0	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	0	1

Table: $AB = \overline{\overline{AB}}$ Typo

The NOR gate is universal

De Morgan's Law

A	B	\bar{A}	\bar{B}	$\bar{A} + \bar{B}$	AB	\overline{AB}
0	0	1	1	1	0	1
0	1	1	0	1	0	1
1	0	0	1	1	0	1
1	1	0	0	0	1	0

Table: $\bar{A} + \bar{B} = \overline{AB}$

AND gate as three NOR gates

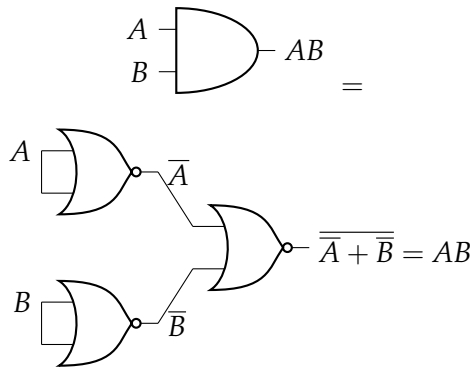


Table of contents

Announcements

Combinational logic

Definitions for more-than-2-input gates

Functional completeness

The set of logic gates {NOT, AND, OR} is universal

The NAND gate is universal

The NOR gate is universal

Basic algorithms for logic simplification