

The basics of logic design

Yipeng Huang

Rutgers University

April 20, 2023

Table of contents

Announcements

Cache-friendly code

- Loop interchange

- Cache blocking

- Multilevel cache hierarchies

- Cache oblivious algorithms

- Memory hierarchy implications for software-hardware abstraction

Transistors: The building block of computers

Combinational logic

- Basic gates

- More-than-2-input gates

Functional completeness

- The set of logic gates {NOT, AND, OR} is universal

- The NAND gate is universal

- The NOR gate is universal

Announcements

Class session plan

- ▶ 4/20, 4/24, 4/27: Diving deeper: Digital logic. (CS:APP Chapter 4.2)
(Recommended reading: Patterson & Hennessy, Computer organization and design, appendix on "The Basics of Logic Design." Available online via Rutgers Libraries)
- ▶ 5/1: Survey of advanced topics in computer architecture.

Table of contents

Announcements

Cache-friendly code

- Loop interchange

- Cache blocking

- Multilevel cache hierarchies

- Cache oblivious algorithms

- Memory hierarchy implications for software-hardware abstraction

Transistors: The building block of computers

Combinational logic

- Basic gates

- More-than-2-input gates

Functional completeness

- The set of logic gates {NOT, AND, OR} is universal

- The NAND gate is universal

- The NOR gate is universal

Cache-friendly code

Algorithms can be written so that they work well with caches

- ▶ Maximize hit rate
- ▶ Minimize miss rate
- ▶ Minimize eviction counts

Do so by:

- ▶ Increasing spatial locality.
- ▶ Increasing temporal locality.

Advanced optimizing compilers can automatically make such optimizations

- ▶ GCC optimizations
- ▶ `https://gcc.gnu.org/onlinedocs/gcc/Optimize-Options.html`
- ▶ `-floop-interchange`
- ▶ `-floop-block`

Loop interchange

Refer to textbook slides on "Rearranging loops to improve spatial locality"

- ▶ Loop interchange increases spatial locality.
- ▶ In PA5, fourth part "cacheBlocking" you can explore the impact of this on matrix multiplication.
- ▶ In practice, programmers do not have to worry about this optimization.
- ▶ Optimized automatically in GCC by compiler flag `-floop-interchange` and `-O3`.

Cache blocking

Refer to textbook slides on "Using blocking to improve temporal locality"

- ▶ Cache blocking increases temporal locality.
- ▶ In PA5, fourth part "cacheBlocking" you can explore the impact of this on matrix multiplication.
- ▶ In practice, programmers do not have to worry about this optimization.
- ▶ Optimized automatically in GCC by compiler flag `-floop-block`. But it is not part of default optimizations such as `-O3` so you have to remember to set it.

Multilevel cache hierarchies

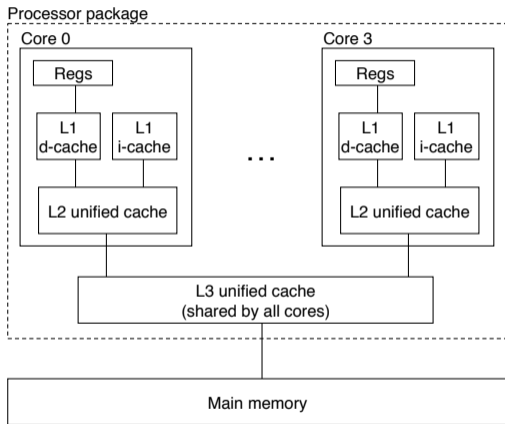


Figure: Intel Core i7 cache hierarchy. Image credit CS:APP

Small fast caches nested inside large slow caches

- ▶ L1 data and instruction cache: 32KB, 64 set, 8-way associative, 64B block, 4 cycle latency.
- ▶ L2 cache: 256KB, 512 set, 8-way associative, 64B block, 10 cycle latency.
- ▶ L3 cache: 8MB, 8192 set, 16-way associative, 64B block, 40-75 cycle latency.

Notice how latency cost increases as E -way associativity increases.

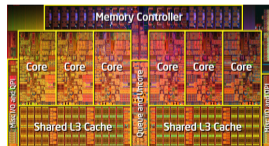


Figure: Intel 2020 Gulftown die shot. Image credit AnandTech

Cache oblivious algorithms

The challenge in writing code / compiling programs to take advantage of caches:

- ▶ Programmers do not easily have information about target machine.
- ▶ Compiling binaries for every envisioned target machine is costly.

Matrix transpose baseline algorithm: iteration

$$\mathbf{A} = \begin{bmatrix} a_{0,0} & a_{0,1} & a_{0,2} & a_{0,3} \\ a_{1,0} & a_{1,1} & a_{1,2} & a_{1,3} \\ a_{2,0} & a_{2,1} & a_{2,2} & a_{2,3} \\ a_{3,0} & a_{3,1} & a_{3,2} & a_{3,3} \end{bmatrix}$$

$$\mathbf{B} = \mathbf{A}^T = \begin{bmatrix} a_{0,0} & a_{1,0} & a_{2,0} & a_{3,0} \\ a_{0,1} & a_{1,1} & a_{2,1} & a_{3,1} \\ a_{0,2} & a_{1,2} & a_{2,2} & a_{3,2} \\ a_{0,3} & a_{1,3} & a_{2,3} & a_{3,3} \end{bmatrix}$$

```
1 for ( size_t i=0; i<n; i++ ) {
2   for ( size_t j=0; j<n; j++ ) {
3     B[ j*n + i ] = A[ i*n + j ];
4   }
5 }
```

Matrix transpose via recursion

$$\mathbf{A} = \begin{bmatrix} A_{0,0} & A_{0,1} \\ A_{1,0} & A_{1,1} \end{bmatrix} = \left[\begin{array}{cc|cc} a_{0,0} & a_{0,1} & a_{0,2} & a_{0,3} \\ a_{1,0} & a_{1,1} & a_{1,2} & a_{1,3} \\ \hline a_{2,0} & a_{2,1} & a_{2,2} & a_{2,3} \\ a_{3,0} & a_{3,1} & a_{3,2} & a_{3,3} \end{array} \right]$$
$$\mathbf{B} = \mathbf{A}^T = \begin{bmatrix} A_{0,0}^T & A_{1,0}^T \\ A_{0,1}^T & A_{1,1}^T \end{bmatrix} = \left[\begin{array}{cc|cc} a_{0,0} & a_{1,0} & a_{2,0} & a_{3,0} \\ a_{0,1} & a_{1,1} & a_{2,1} & a_{3,1} \\ \hline a_{0,2} & a_{1,2} & a_{2,2} & a_{3,2} \\ a_{0,3} & a_{1,3} & a_{2,3} & a_{3,3} \end{array} \right]$$

Strategy:

- ▶ Divide and conquer large matrix to transpose into smaller transpositions.
- ▶ After some recursion, problem will fit well inside cache capacity.
- ▶ Once enough locality exists withing subroutine, switch to plain iterative approach.

Advantages:

- ▶ No need to know about cache capacity and parameters beforehand.
- ▶ Works well with deep multilevel cache hierarchies: different amounts of locality for each cache level.

Memory hierarchy implications for software-hardware abstraction

It is not entirely true the architecture can hide details of microarchitecture

Even less true going forward. What to do?

Application level recommendations

- ▶ Use industrial strength, optimized libraries compiled for target machine.
- ▶ Lapack, Linpack, Matlab, Python SciPy, NumPy...
- ▶ <https://people.inf.ethz.ch/markusp/teaching/263-2300-ETH-spring11/slides/class08.pdf>

Algorithm level recommendations

Deploy cache-oblivious algorithm implementations.

Compiler level recommendations

- ▶ Enable compiler optimizations—*e.g.*, `-O3`, `-floop-interchange`, `-floop-block`.
- ▶ <https://gcc.gnu.org/onlinedocs/gcc/Optimize-Options.html>

Table of contents

Announcements

Cache-friendly code

- Loop interchange

- Cache blocking

- Multilevel cache hierarchies

- Cache oblivious algorithms

- Memory hierarchy implications for software-hardware abstraction

Transistors: The building block of computers

Combinational logic

- Basic gates

- More-than-2-input gates

Functional completeness

- The set of logic gates {NOT, AND, OR} is universal

- The NAND gate is universal

- The NOR gate is universal


Computer organization

Layer cake

- ▶ Society
- ▶ Human beings
- ▶ Applications
- ▶ Algorithms
- ▶ High-level programming languages
- ▶ Interpreters
- ▶ Low-level programming languages
- ▶ Compilers
- ▶ Architectures
- ▶ Microarchitectures
- ▶ Sequential/combinational logic
- ▶ Transistors
- ▶ Semiconductors
- ▶ Materials science

Everything is bits

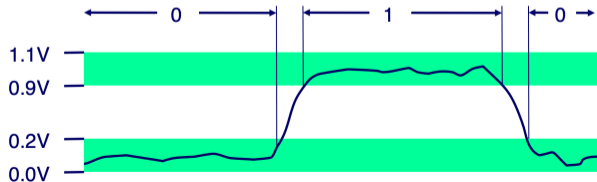- Each bit is 0 or 1
- By encoding/interpreting sets of bits in various ways
 - Computers determine what to do (instructions)
 - ... and represent and manipulate numbers, sets, strings, etc...
- Why bits? **Electronic Implementation**
 - Easy to store with bistable elements
 - Reliably transmitted on noisy and inaccurate wires




To build logic, we need switches

Vacuum tubes a.k.a. valves



Figure: Source: By Stefan Riepl (Quark48) - Self-photographed, CC BY-SA 2.0
<https://commons.wikimedia.org/w/index.php?curid=14682022>

Transistors

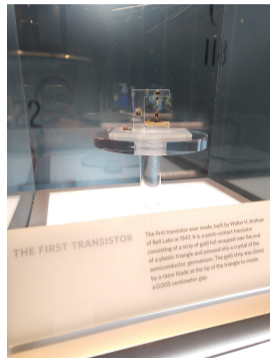

- ▶ The first transistor. Developed at Bell Labs, Murray Hill, New Jersey
- ▶ <https://www.bell-labs.com/about/locations/>

MOSFETs

MOS: Metal-oxide-semiconductor

- ▶ A sandwich of conductor-insulator-semiconductor.

FET: Field-effect transistor

- ▶ Gate exerts electric field that changes conductivity of semiconductor.

NMOS, PMOS, CMOS

PMOS: P-type MOS

- ▶ positive gate voltage, acts as open circuit (insulator)
- ▶ negative gate voltage, acts as short circuit (conductor)

NMOS: N-type MOS

- ▶ positive gate voltage, acts as short circuit (conductor)
- ▶ negative gate voltage, acts as open circuit (insulator)

CMOS: Complementary MOS

- ▶ A combination of NMOS and PMOS to build logical gates such as NOT, AND, OR.
- ▶ We'll go to slides posted in supplementary material to see how they work.

Combinational vs. sequential logic

Combinational logic

- ▶ No internal state nor memory
- ▶ Output depends entirely on input
- ▶ Examples: NOT, AND, NAND, OR, NOR, XOR, XNOR gates, decoders, multiplexers.

Sequential logic

- ▶ Has internal state (memory)
- ▶ Output depends on the inputs and also internal state
- ▶ Examples: latches, flip-flops, Mealy and Moore machines, registers, pipelines, SRAMs.

Table of contents

Announcements

Cache-friendly code

- Loop interchange

- Cache blocking

- Multilevel cache hierarchies

- Cache oblivious algorithms

- Memory hierarchy implications for software-hardware abstraction

Transistors: The building block of computers

Combinational logic

- Basic gates

- More-than-2-input gates


Functional completeness

- The set of logic gates {NOT, AND, OR} is universal

- The NAND gate is universal

- The NOR gate is universal


NOT gate

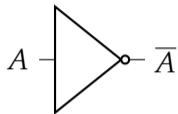

A	\bar{A}
0	1
1	0


Table: Truth table for NOT gate

AND gate, NAND gate

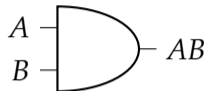

<i>A</i>	<i>B</i>	<i>AB</i>
0	0	0
0	1	0
1	0	0
1	1	1


Table: Truth table for AND gate

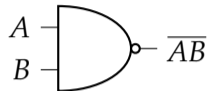

<i>A</i>	<i>B</i>	\overline{AB}
0	0	1
0	1	1
1	0	1
1	1	0


Table: Truth table for NAND gate

OR gate, NOR gate

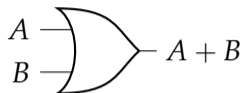

A	B	$A + B$
0	0	0
0	1	1
1	0	1
1	1	1


Table: Truth table for OR gate

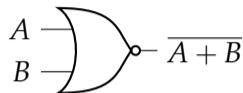

A	B	$\overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0


Table: Truth table for NOR gate

XOR gate, XNOR gate

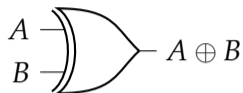

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0


Table: Truth table for XOR gate

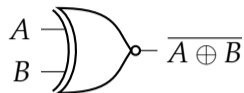

A	B	$\overline{A \oplus B}$
0	0	1
0	1	0
1	0	0
1	1	1

Table: Truth table for XNOR gate



More-than-2-input AND gate

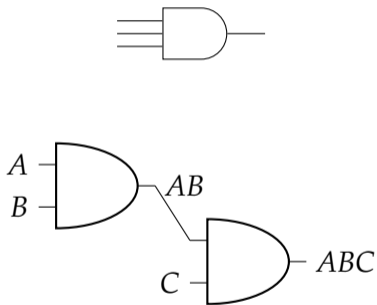

<i>A</i>	<i>B</i>	<i>C</i>	<i>ABC</i>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Table: Truth table for three-input AND gate

More-than-2-input OR gate

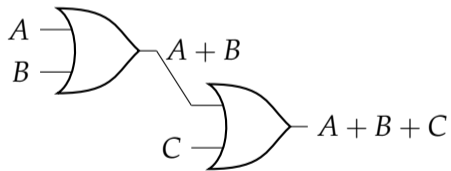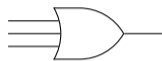

A	B	C	$A + B + C$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Table: Truth table for three-input OR gate

Table of contents

Announcements

Cache-friendly code

- Loop interchange

- Cache blocking

- Multilevel cache hierarchies

- Cache oblivious algorithms

- Memory hierarchy implications for software-hardware abstraction

Transistors: The building block of computers

Combinational logic

- Basic gates

- More-than-2-input gates

Functional completeness

- The set of logic gates {NOT, AND, OR} is universal

- The NAND gate is universal

- The NOR gate is universal

The set of logic gates {NOT, AND, OR} is universal

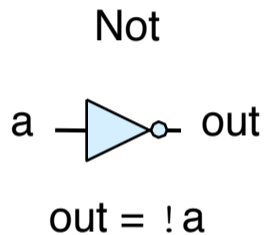
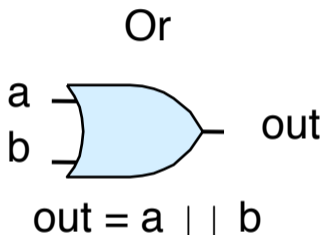
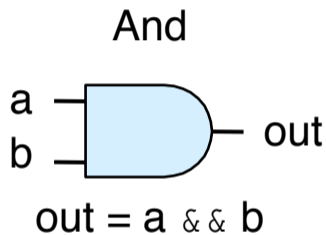


Figure: Source: CS:APP

The set of logic gates {NOT, AND, OR} is universal


- ▶ Any truth table can be expressed as sum of products form.
- ▶ Write each row with output 1 as a product (minterm).
- ▶ Sum the products (minterm).
- ▶ Forms a disjunctive normal form (DNF).
- ▶ $D = \bar{A}\bar{B}\bar{C} + A\bar{B}C$
- ▶ Always only needs NOT, AND, OR gates.
- ▶ Supplementary slides example...

Logical Completeness

Can implement ANY truth table with AND, OR, NOT.

A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

Sum of products
OR of AND clauses

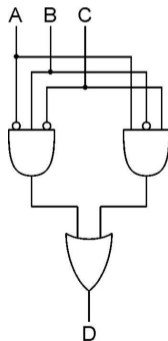

1. AND combinations that yield a "1" in the truth table.

2. OR the results of the AND gates.

The set of logic gates {NOT, AND, OR} is universal

- ▶ Any truth table can be expressed as sum of products form.
- ▶ Write each row with output 1 as a product (minterm).
- ▶ Sum the products (minterm).
- ▶ Forms a disjunctive normal form (DNF).
- ▶ $D = \bar{A}B\bar{C} + A\bar{B}C$
- ▶ Always only needs NOT, AND, OR gates.
- ▶ Supplementary slides example...


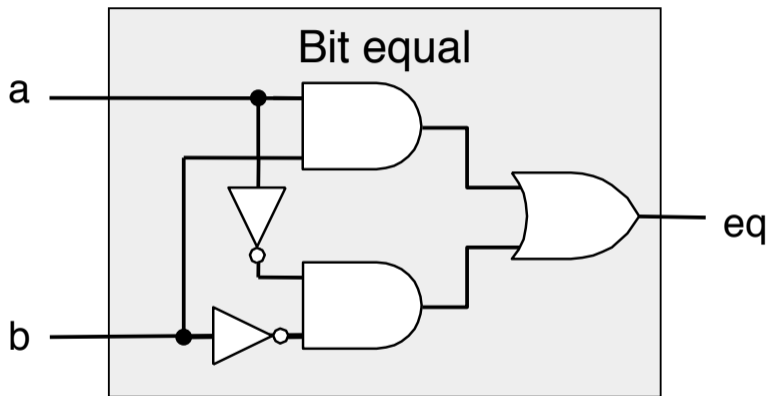


Figure: Source: CS:APP

The NAND gate is universal


NOT gate as a single NAND gate

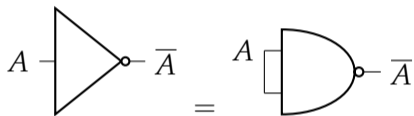

A	\bar{A}	AA	\overline{AA}
0	1	0	1
1	0	1	0

Table: $\bar{A} = \overline{AA}$

AND gate as two NAND gates

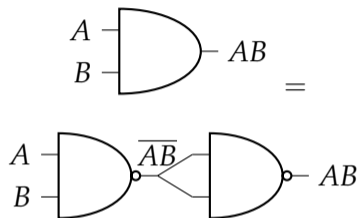

A	B	AB	\overline{AB}	$\overline{\overline{AB}}$
0	0	0	1	0
0	1	0	1	0
1	0	0	1	0
1	1	1	0	1

Table: $AB = \overline{\overline{AB}}$



The NAND gate is universal

De Morgan's Law

A	B	\bar{A}	\bar{B}	$\bar{A}\bar{B}$	$A + B$	$\overline{\bar{A}\bar{B}}$
0	0	1	1	1	0	1
0	1	1	0	0	1	0
1	0	0	1	0	1	0
1	1	0	0	0	1	0


Table: $\bar{A}\bar{B} = \overline{A + B}$

OR gate as three NAND gates

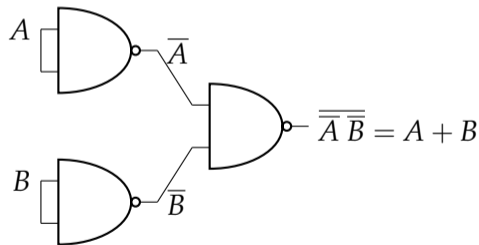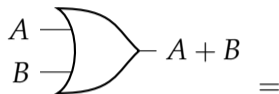

The NOR gate is universal


NOT gate as a single NOR gate

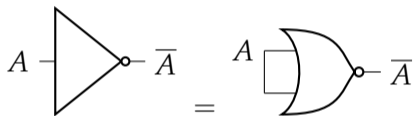

A	\bar{A}	$A + A$	$\overline{A + A}$
0	1	0	1
1	0	1	0

Table: $\bar{A} = \overline{A + A}$

OR gate as two NOR gates

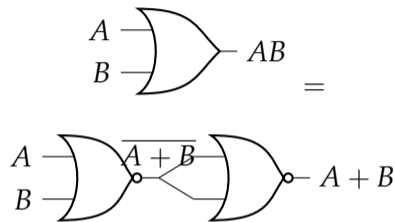

A	B	$A + B$	$\overline{A + B}$	$\overline{\overline{A + B}}$
0	0	0	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	0	1

Table: $A + B = \overline{\overline{A + B}}$

The NOR gate is universal

De Morgan's Law

A	B	\bar{A}	\bar{B}	$\bar{A} + \bar{B}$	AB	\overline{AB}
0	0	1	1	1	0	1
0	1	1	0	1	0	1
1	0	0	1	1	0	1
1	1	0	0	0	1	0

Table: $\bar{A} + \bar{B} = \overline{AB}$

AND gate as three NOR gates

