

# The basics of logic design: Sequential logic

Yipeng Huang

Rutgers University

April 27, 2023

# Table of contents

Announcements

Combinational logic

Decoders

Multiplexers

PA6 Demo code: directMapped read logic

Sequential logic

SR latch

SRAM cell

# Announcements

## Class session plan

- ▶ Thursday, 4/27: Diving deeper: Digital logic. (CS:APP Chapter 4.2) (Recommended reading: Patterson & Hennessy, Computer organization and design, appendix on "The Basics of Logic Design." Available online via Rutgers Libraries)
- ▶ Monday, 5/1: Survey of advanced topics in computer architecture.
- ▶ Thursday, 5/4: 8:00-11:00 AM, Hill 114, closed book, closed notes, no electronic devices, no calculator final exam.

# Combinational vs. sequential logic

## Combinational logic

- ▶ No internal state nor memory
- ▶ Output depends entirely on input
- ▶ Examples: NOT, AND, NAND, OR, NOR, XOR, XNOR gates, decoders, multiplexers.

## Sequential logic

- ▶ Has internal state (memory)
- ▶ Output depends on the inputs and also internal state
- ▶ Examples: latches, flip-flops, Mealy and Moore machines, registers, pipelines, SRAMs.

# Table of contents

Announcements

Combinational logic

Decoders

Multiplexers

PA6 Demo code: directMapped read logic

Sequential logic

SR latch

SRAM cell

# Decoders

Takes  $n$ -bit input, uses it as an index to enable exactly one of  $2^n$  outputs

## Internal design of 1:2 decoder

---

 


Figure: Source: Mano & Kime

# Decoders

## Hierarchical design of decoder (2:4 decoder)

Takes n-bit input, uses it as an index to enable exactly one of  $2^n$  outputs

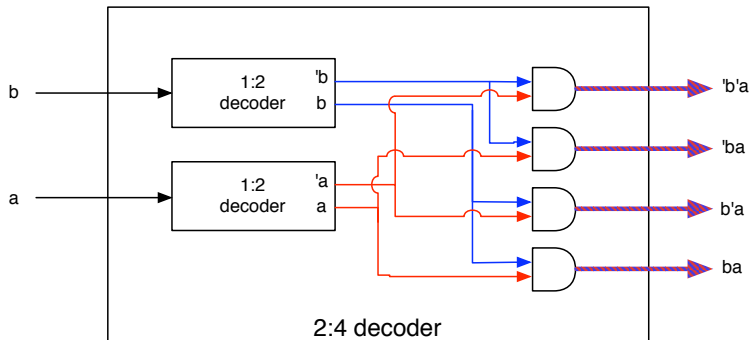



Figure: Source: Mano & Kime

# Decoders
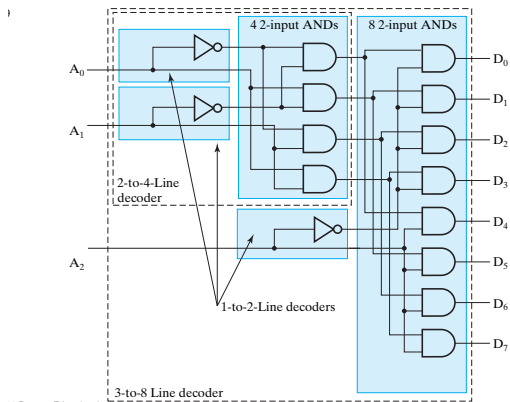
## Decoder (3:8)

Takes n-bit input, uses it as an index to enable exactly one of  $2^n$  outputs

Hierarchical design: use small decoders to build bigger decoder



Note:  $A_2$  "selects" whether the 2-to-4 line decoder is active in the top half ( $A_2=0$ ) or the bottom ( $A_2=1$ )

Figure: Source: Mano & Kime



# Multiplexers

Using n-bit selector input, select among one of  $2^n$  choices

 


Figure: Source: CS:APP

# Multiplexers

Using n-bit selector input, select among one of  $2^n$  choices

 



Figure: Source: CS:APP

# Multiplexers
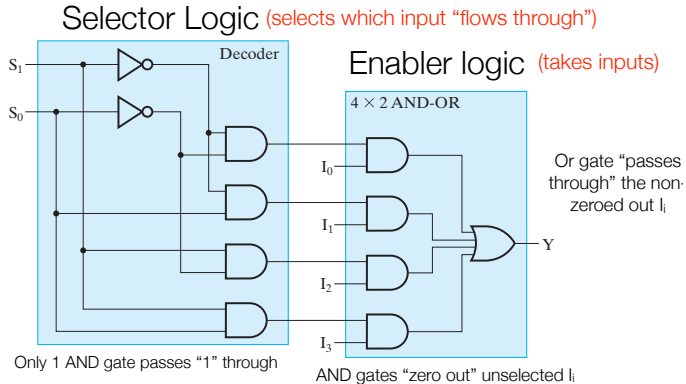
## Internal mux organization

3-26

Using n-bit selector input, select among one of  $2^n$  choices



© 2008 Pearson Education, Inc.  
M. Morris Mano & Charles R. Kime  
LOGIC AND COMPUTER DESIGN FUNDAMENTALS, 4e

Figure: Source: Mano & Kime

# Table of contents

Announcements

Combinational logic

Decoders

Multiplexers

PA6 Demo code: directMapped read logic

Sequential logic

SR latch

SRAM cell

# directMapped read logic

# Table of contents

Announcements

Combinational logic

Decoders

Multiplexers

PA6 Demo code: directMapped read logic

Sequential logic

SR latch

SRAM cell

## Sequential logic

 


Figure: Source: Mano & Kime

# The simplest sequential logic element: The set/reset (SR) latch

## SR latch

- Latch constructed of cross-coupled NOR gates


 


Figure: Source: Mano & Kime

 

# The simplest sequential logic element: The set/reset (SR) latch

SR latch



R	S	Q	$\overline{Q}$
0	0	Q	$\overline{Q}$
0	1	1	0
1	0	0	1
1	1		

Hold previous value

Figure: Source: Mano & Kime

# 6 transistor SRAM cell


 


Figure: Source: Wikimedia

# Asynchronous / Synchronous circuits

## Timing

Circuit:

 

Voltages over time:

