

# The basics of logic design: Combinational logic

Yipeng Huang

Rutgers University

April 18, 2024

# Table of contents

Announcements

Transistors: The building block of computers

Combinational logic

Basic gates

More-than-2-input gates

Functional completeness

The set of logic gates {NOT, AND, OR} is universal

The NAND gate is universal

The NOR gate is universal

Combinational logic

Decoders

Multiplexers

PA6 Demo code: directMapped read logic

# Announcements

## Class session plan

- ▶ Thursday, 4/18 & Tuesday, 4/23: Diving deeper: Digital logic. (CS:APP Chapter 4.2) (Recommended reading: Patterson & Hennessy, Computer organization and design, appendix on "The Basics of Logic Design." Available online via Rutgers Libraries)
- ▶ Thursday, 4/25: Survey of advanced topics in computer architecture.
- ▶ Tuesday, 5/7: 12:00-15:00, SERC 111, closed book, closed notes, no electronic devices, no calculator final exam.

# Table of contents

Announcements

Transistors: The building block of computers

Combinational logic

Basic gates

More-than-2-input gates

Functional completeness

The set of logic gates {NOT, AND, OR} is universal

The NAND gate is universal

The NOR gate is universal

Combinational logic

Decoders

Multiplexers

PA6 Demo code: directMapped read logic


# Computer organization

## Layer cake

- ▶ Society
- ▶ Human beings
- ▶ Applications
- ▶ Algorithms
- ▶ High-level programming languages
- ▶ Interpreters
- ▶ Low-level programming languages
- ▶ Compilers
- ▶ Architectures
- ▶ Microarchitectures
- ▶ Sequential/combinational logic
- ▶ Transistors
- ▶ Semiconductors
- ▶ Materials science
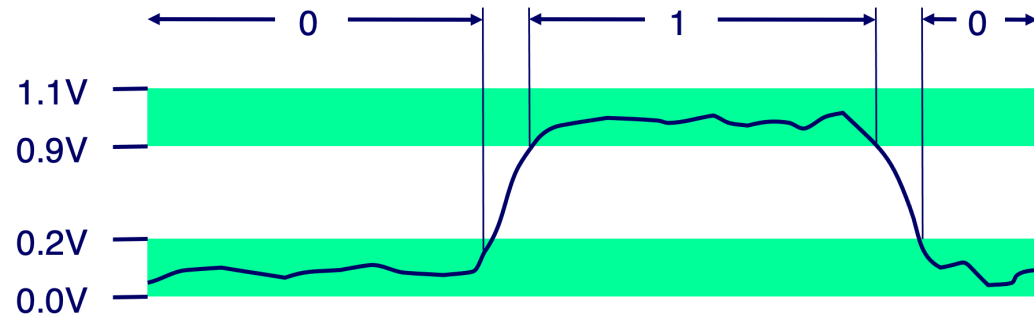
## Everything is bits

- **Each bit is 0 or 1**
- **By encoding/interpreting sets of bits in various ways**
  - Computers determine what to do (instructions)
  - ... and represent and manipulate numbers, sets, strings, etc...
- **Why bits? Electronic Implementation**
  - Easy to store with bistable elements
  - Reliably transmitted on noisy and inaccurate wires



# To build logic, we need switches


## Vacuum tubes a.k.a. valves



**Figure:** Source: By Stefan Riepl (Quark48) - Self-photographed, CC BY-SA 2.0

<https://commons.wikimedia.org/w/index.php?curid=14682022>

## Transistors

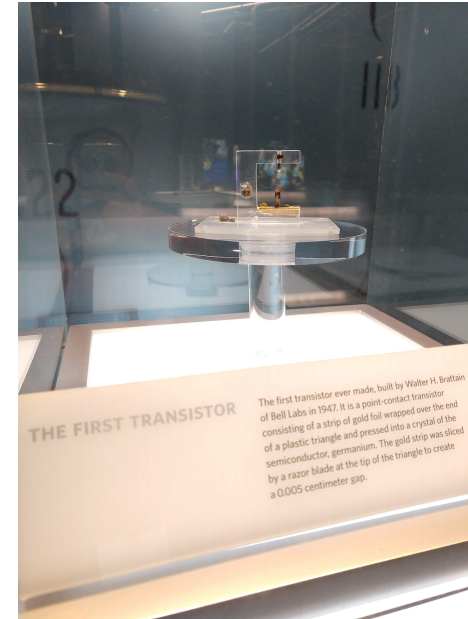

- ▶ The first transistor. Developed at Bell Labs, Murray Hill, New Jersey
- ▶ <https://www.bell-labs.com/about/locations/>

# MOSFETs

transistors { BJT  
MOSFETs

MOS: Metal-oxide-semiconductor

- ▶ A sandwich of conductor-insulator-semiconductor.

FET: Field-effect transistor

- ▶ Gate exerts electric field that changes conductivity of semiconductor.



# NMOS, PMOS, CMOS

## PMOS: P-type MOS

- ▶ positive gate voltage, acts as open circuit (insulator)
- ▶ negative gate voltage, acts as short circuit (conductor)

## NMOS: N-type MOS

- ▶ positive gate voltage, acts as short circuit (conductor)
- ▶ negative gate voltage, acts as open circuit (insulator)

## CMOS: Complementary MOS

- ▶ A combination of NMOS and PMOS to build logical gates such as NOT, AND, OR.
- ▶ We'll go to slides posted in supplementary material to see how they work.

# Combinational vs. sequential logic

## Combinational logic

- ▶ No internal state nor memory
- ▶ Output depends entirely on input
- ▶ Examples: NOT, AND, NAND, OR, NOR, XOR, XNOR gates, decoders, multiplexers.

## Sequential logic

- ▶ Has internal state (memory)
- ▶ Output depends on the inputs and also internal state
- ▶ Examples: latches, flip-flops, Mealy and Moore machines, registers, pipelines, SRAMs.

# Table of contents

Announcements

Transistors: The building block of computers

Combinational logic

Basic gates

More-than-2-input gates

Functional completeness

The set of logic gates {NOT, AND, OR} is universal

The NAND gate is universal

The NOR gate is universal


Combinational logic

Decoders

Multiplexers

PA6 Demo code: directMapped read logic


# NOT gate

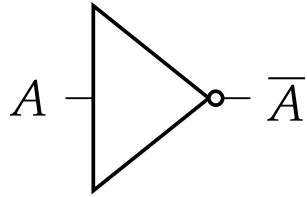

$A$	$\bar{A}$
0	1
1	0


**Table:** Truth table for NOT gate

# AND gate, NAND gate

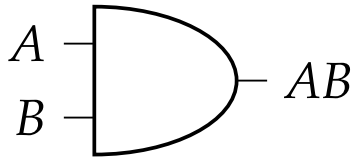

$A$	$B$	$AB$
0	0	0
0	1	0
1	0	0
1	1	1


Table: Truth table for AND gate

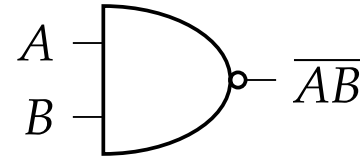

$A$	$B$	$\overline{AB}$
0	0	1
0	1	1
1	0	1
1	1	0


Table: Truth table for NAND gate

# OR gate, NOR gate

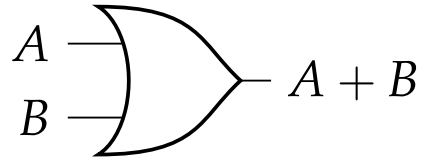

A	B	A + B
0	0	0
0	1	1
1	0	1
1	1	1


Table: Truth table for OR gate

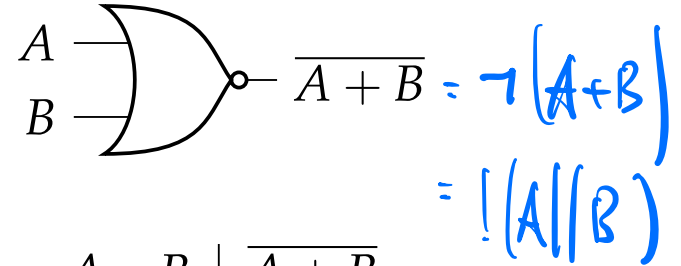

A	B	$\overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0


Table: Truth table for NOR gate

# XOR gate, XNOR gate

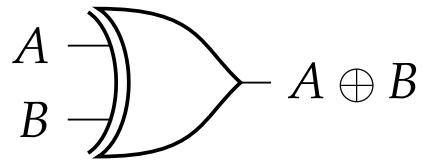

$A$	$B$	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0


Table: Truth table for XOR gate

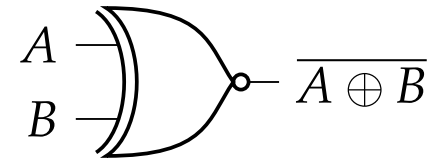

$A$	$B$	$\overline{A \oplus B}$
0	0	1
0	1	0
1	0	0
1	1	1

Table: Truth table for XNOR gate

# More-than-2-input AND gate

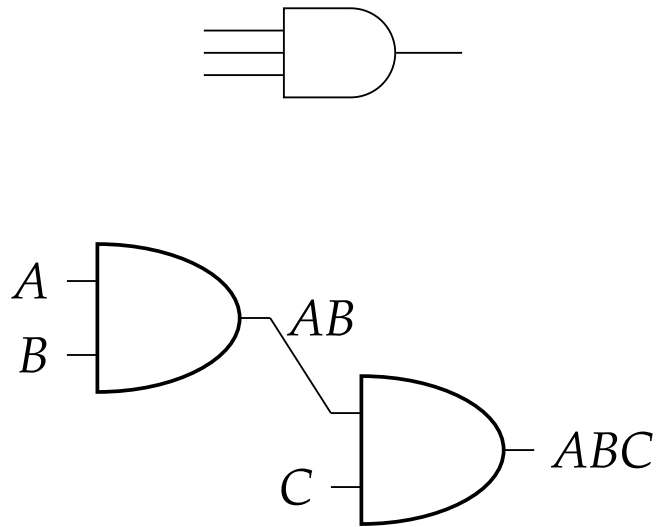


$A$	$B$	$C$	$ABC$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Table: Truth table for three-input AND gate



# More-than-2-input OR gate

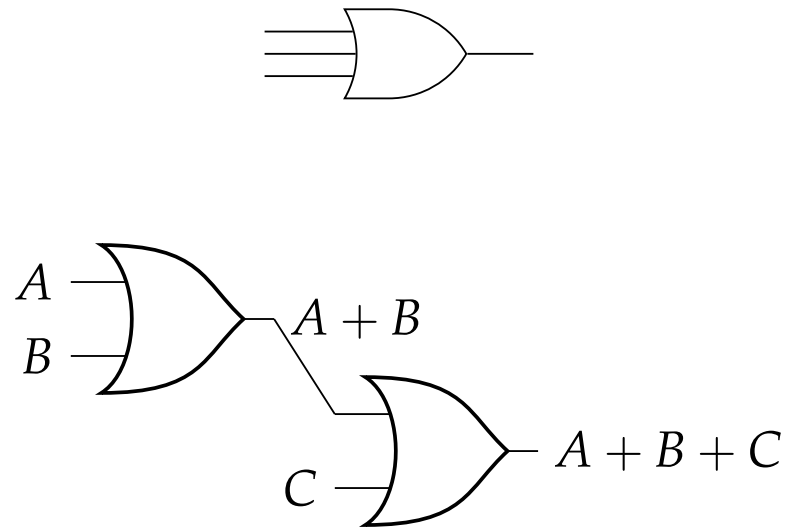

$A$	$B$	$C$	$A + B + C$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Table: Truth table for three-input OR gate

# Table of contents

Announcements

Transistors: The building block of computers

Combinational logic

Basic gates

More-than-2-input gates

Functional completeness

The set of logic gates {NOT, AND, OR} is universal

The NAND gate is universal

The NOR gate is universal

Combinational logic

Decoders

Multiplexers

PA6 Demo code: directMapped read logic

# The set of logic gates {NOT, AND, OR} is universal

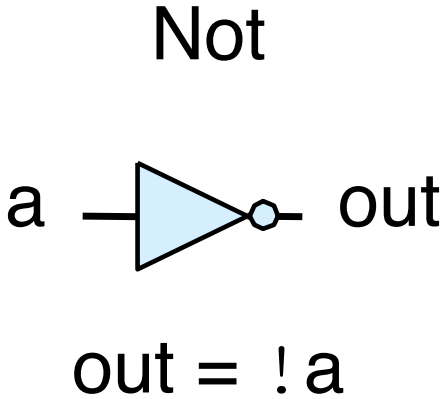
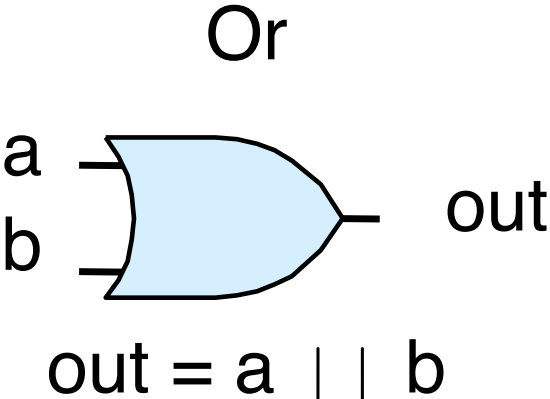
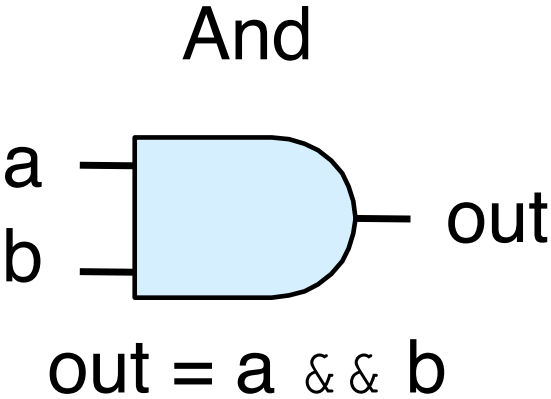


Figure: Source: CS:APP

# The set of logic gates {NOT, AND, OR} is universal

B XOR (A and C)


## Logical Completeness

- ▶ Any truth table can be expressed as sum of products form.
- ▶ Write each row with output 1 as a product (minterm).
- ▶ Sum the products (minterm).
- ▶ Forms a disjunctive normal form (DNF).
- ▶  $D = \bar{A}\bar{B}C + A\bar{B}C$
- ▶ Always only needs NOT, AND, OR gates.
- ▶ Supplementary slides example...

Can implement ANY truth table with AND, OR, NOT.

A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

Sum of products  
OR of AND clauses

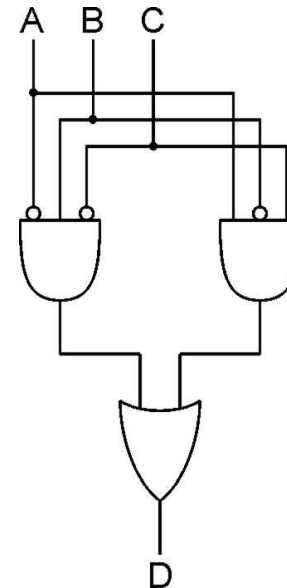

1. AND combinations that yield a "1" in the truth table.

2. OR the results of the AND gates.

# The set of logic gates {NOT, AND, OR} is universal

- ▶ Any truth table can be expressed as sum of products form.
- ▶ Write each row with output 1 as a product (minterm).
- ▶ Sum the products (minterm).
- ▶ Forms a disjunctive normal form (DNF).
- ▶  $D = \bar{A}B\bar{C} + A\bar{B}C$
- ▶ Always only needs NOT, AND, OR gates.
- ▶ Supplementary slides example...


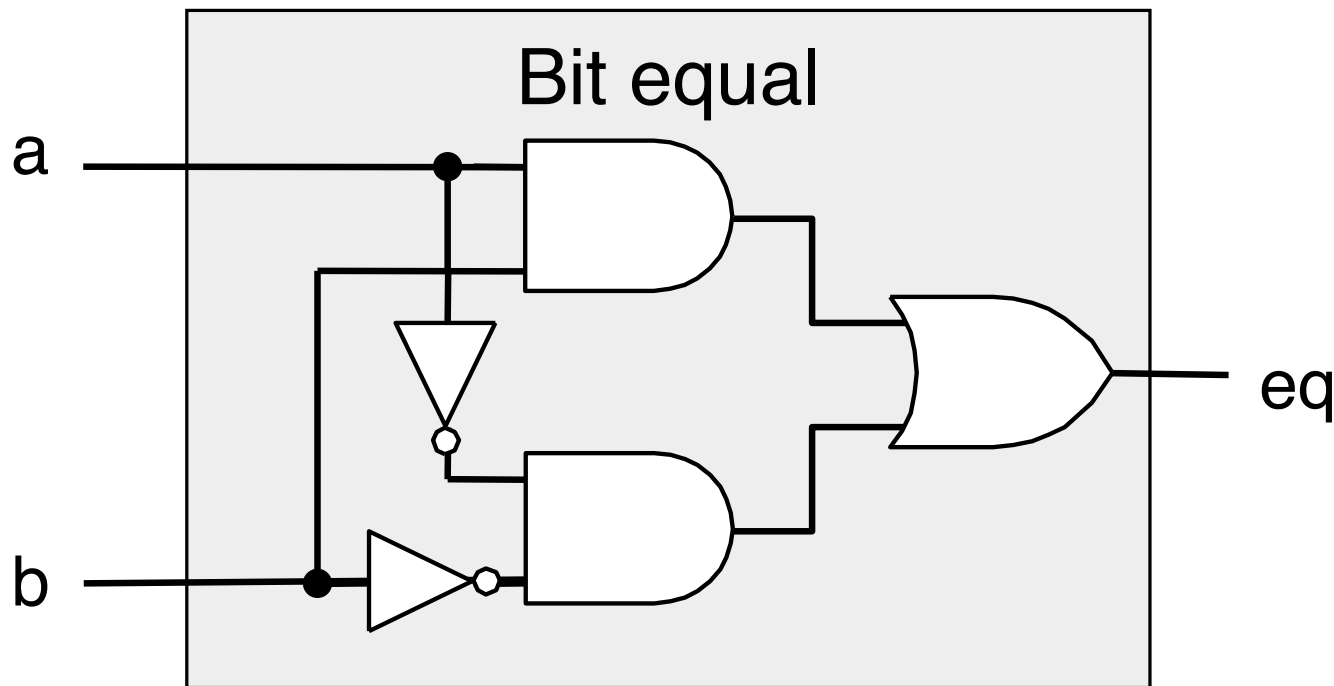


Figure: Source: CS:APP

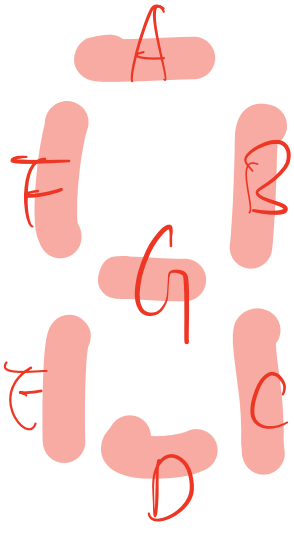


num	$n(z)$	$n(z)$	$n(z)$	$n(0)$	C
0	0	0	0	0	H
1	0	0	0	0	H
2	0	0	0	0	H
3	0	0	0	0	H
4	0	0	0	0	H
5	0	0	0	0	H
6	0	0	0	0	H
7	0	0	0	0	H
8	0	0	0	0	H
9	0	0	0	0	H

$$\bar{C} = \bar{n}(z) \vee \bar{n}(z) \vee \bar{n}(z) \vee \bar{n}(0)$$

# The NAND gate is universal


## NOT gate as a single NAND gate

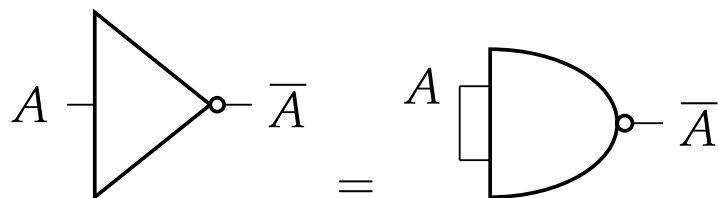

$A$	$\bar{A}$	$AA$	$\overline{AA}$
0	1	0	1
1	0	1	0

Table:  $\bar{A} = \overline{AA}$

## AND gate as two NAND gates

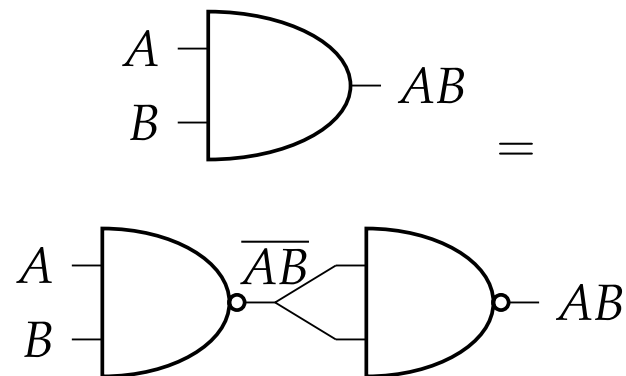

$A$	$B$	$AB$	$\overline{AB}$	$\overline{\overline{AB}}$
0	0	0	1	0
0	1	0	1	0
1	0	0	1	0
1	1	1	0	1

Table:  $AB = \overline{\overline{AB}}$



# The NAND gate is universal

## De Morgan's Law

$A$	$B$	$\bar{A}$	$\bar{B}$	$\bar{A}\bar{B}$	$A + B$	$\overline{A + B}$
0	0	1	1	1	0	1
0	1	1	0	0	1	0
1	0	0	1	0	1	0
1	1	0	0	0	1	0

Table:  $\bar{A}\bar{B} = \overline{A + B}$


## OR gate as three NAND gates

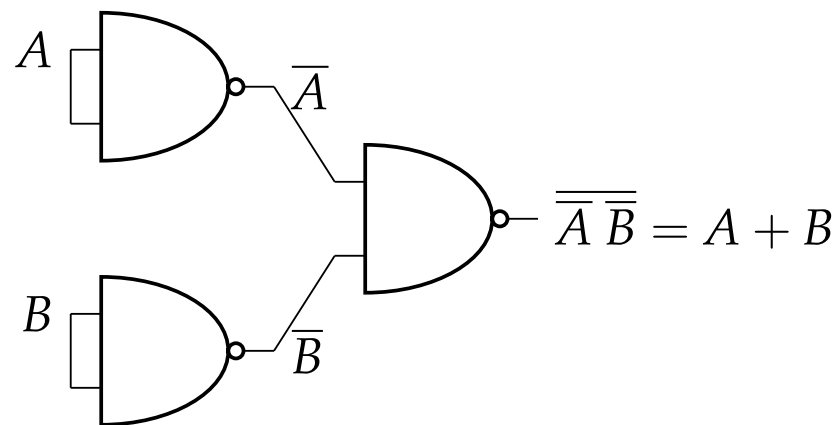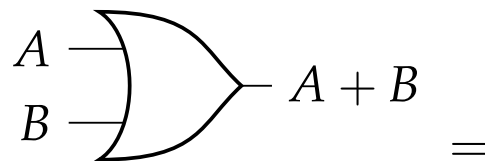



# The NOR gate is universal


## NOT gate as a single NOR gate

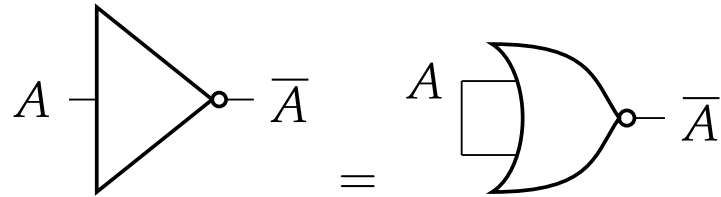

$A$	$\bar{A}$	$A + A$	$\overline{A + A}$
0	1	0	1
1	0	1	0

Table:  $\bar{A} = \overline{A + A}$

## OR gate as two NOR gates

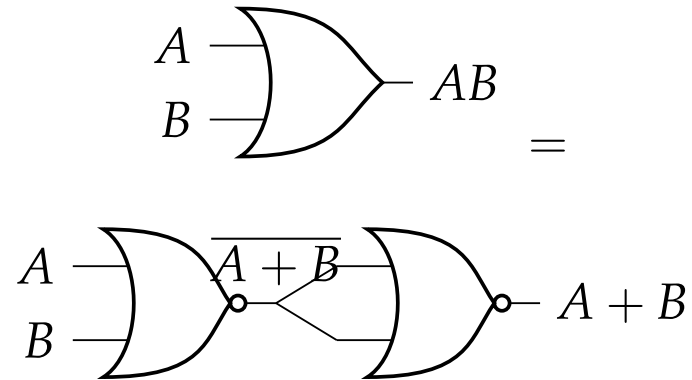

$A$	$B$	$A + B$	$\overline{A + B}$	$\overline{\overline{A + B}}$
0	0	0	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	0	1

Table:  $A + B = \overline{\overline{A + B}}$



# The NOR gate is universal

## De Morgan's Law

$A$	$B$	$\bar{A}$	$\bar{B}$	$\bar{A} + \bar{B}$	$AB$	$\overline{AB}$
0	0	1	1	1	0	1
0	1	1	0	1	0	1
1	0	0	1	1	0	1
1	1	0	0	0	1	0

Table:  $\bar{A} + \bar{B} = \overline{AB}$

## AND gate as three NOR gates

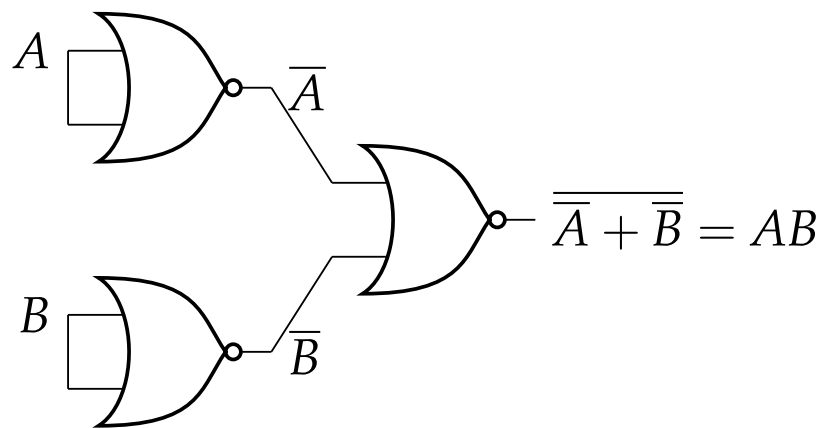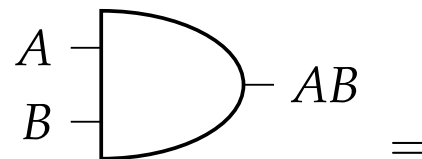

# Combinational vs. sequential logic

## Combinational logic

- ▶ No internal state nor memory
- ▶ Output depends entirely on input
- ▶ Examples: NOT, AND, NAND, OR, NOR, XOR, XNOR gates, decoders, multiplexers.

## Sequential logic

- ▶ Has internal state (memory)
- ▶ Output depends on the inputs and also internal state
- ▶ Examples: latches, flip-flops, Mealy and Moore machines, registers, pipelines, SRAMs.

# Table of contents

Announcements

Transistors: The building block of computers

Combinational logic

Basic gates

More-than-2-input gates

Functional completeness

The set of logic gates {NOT, AND, OR} is universal

The NAND gate is universal

The NOR gate is universal

Combinational logic

Decoders

Multiplexers

PA6 Demo code: directMapped read logic

# Decoders

Takes  $n$ -bit input, uses it as an index to enable exactly one of  $2^n$  outputs

## Internal design of 1:2 decoder

---

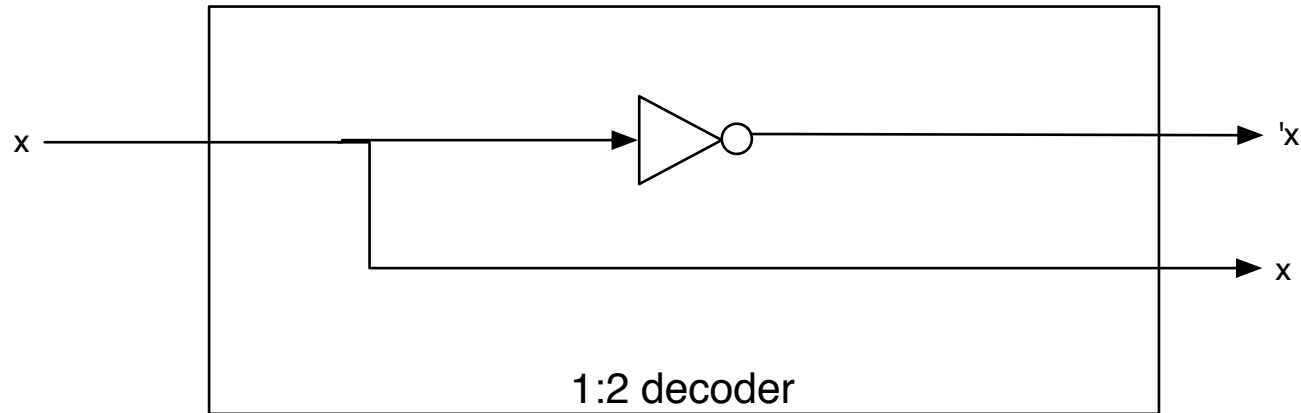


Figure: Source: Mano & Kime

# Decoders

## Hierarchical design of decoder (2:4 decoder)

Takes  $n$ -bit input, uses it as an index to enable exactly one of  $2^n$  outputs


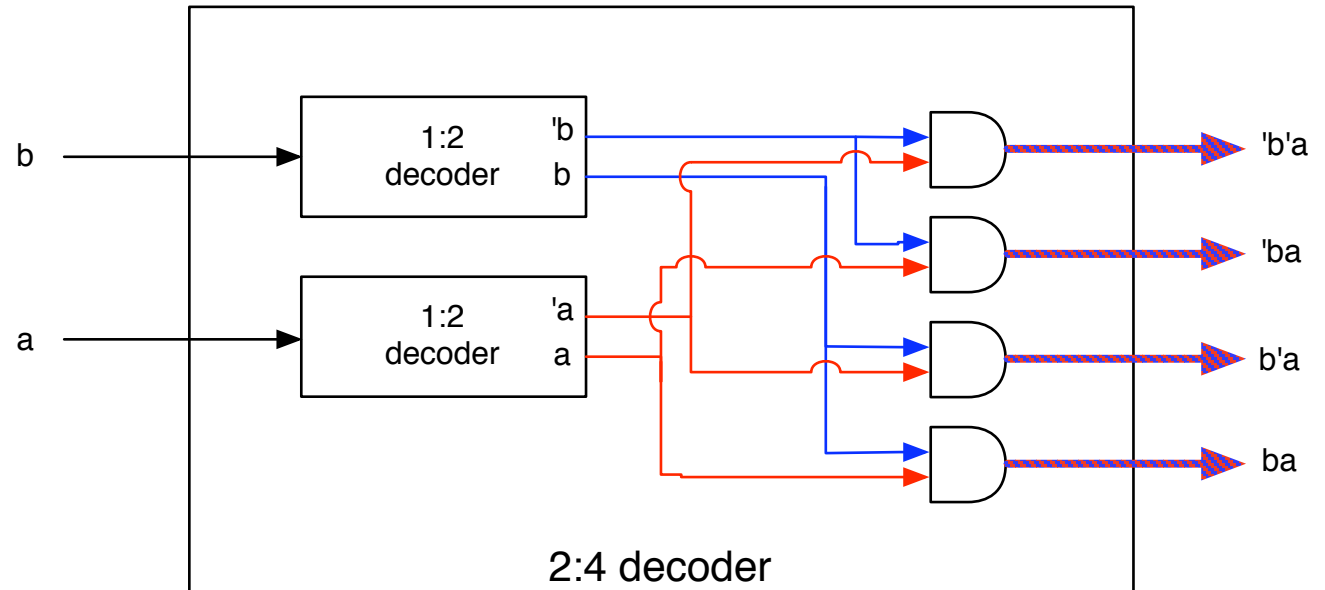


Figure: Source: Mano & Kime

# Decoders
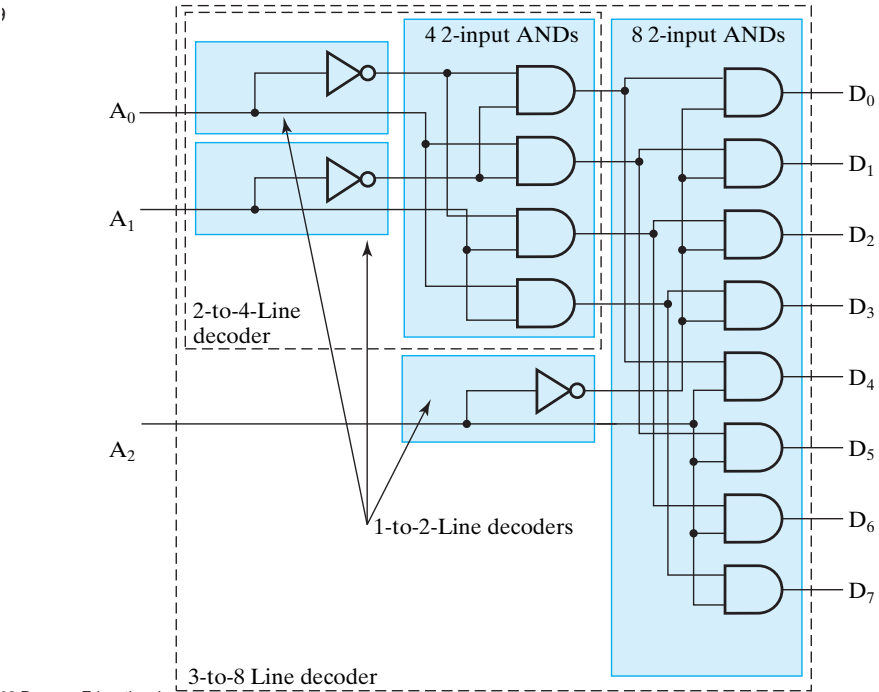
## Decoder (3:8)

Hierarchical design: use small decoders to build bigger decoder



Takes  $n$ -bit input, uses it as an index to enable exactly one of  $2^n$  outputs

Note:  $A_2$  “selects” whether the 2-to-4 line decoder is active in the top half ( $A_2=0$ ) or the bottom ( $A_2=1$ )

Figure: Source: Mano & Kime

# Multiplexers

Using n-bit selector input, select among one of  $2^n$  choices

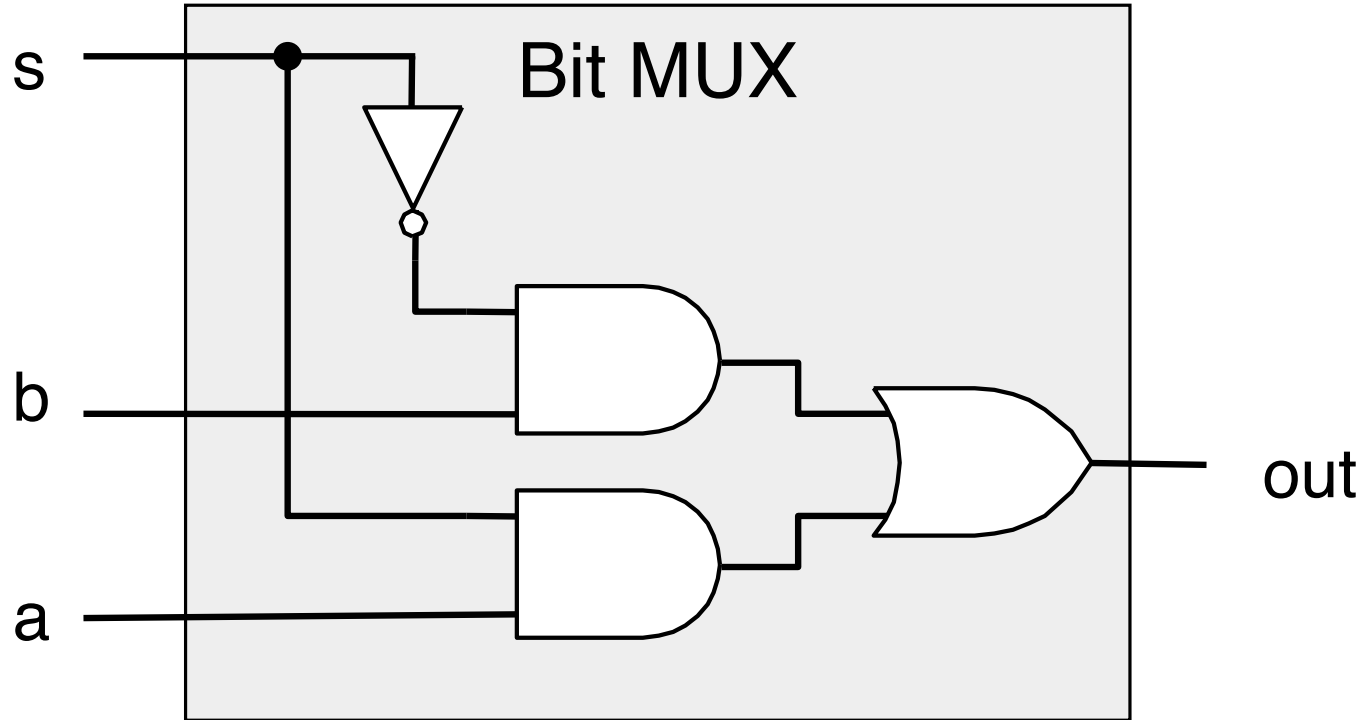


Figure: Source: CS:APP



# Multiplexers

Using n-bit selector input, select among one of  $2^n$  choices

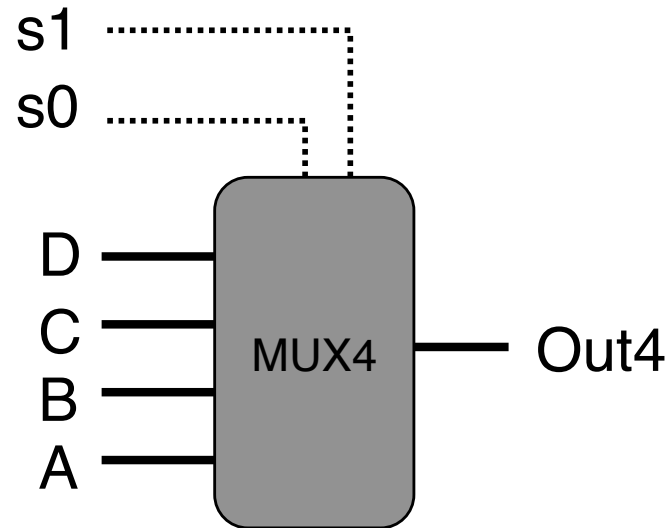



Figure: Source: CS:APP

# Multiplexers
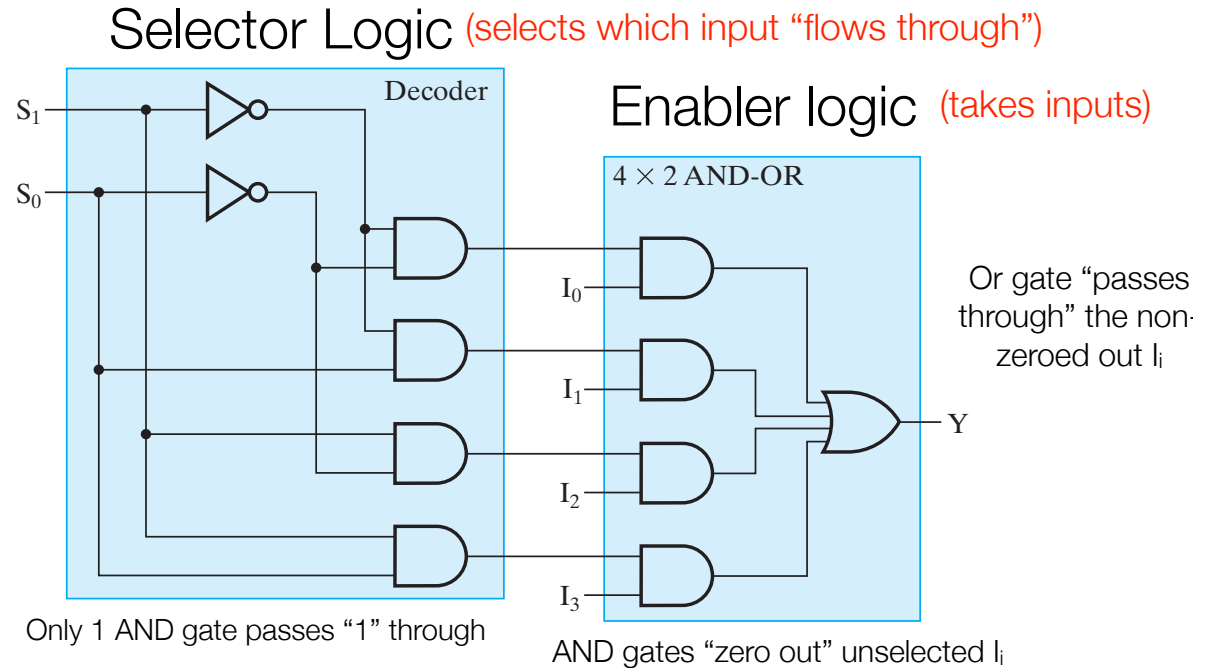
## Internal mux organization

3-26

Using  $n$ -bit selector input, select among one of  $2^n$  choices



© 2008 Pearson Education, Inc.  
M. Morris Mano & Charles R. Kime  
LOGIC AND COMPUTER DESIGN FUNDAMENTALS, 4e

Figure: Source: Mano & Kime

# Table of contents

Announcements

Transistors: The building block of computers

Combinational logic

Basic gates

More-than-2-input gates

Functional completeness

The set of logic gates {NOT, AND, OR} is universal

The NAND gate is universal

The NOR gate is universal

Combinational logic

Decoders

Multiplexers

PA6 Demo code: directMapped read logic

# directMapped read logic