

# The basics of logic design: Sequential logic

Yipeng Huang

Rutgers University

April 23, 2024

# Table of contents

## Announcements

## Functional completeness

The set of logic gates {NOT, AND, OR} is universal

The NAND gate is universal

The NOR gate is universal

## Combinational logic

Decoders

Multiplexers

## PA6 Demo code: directMapped read logic

## Sequential logic

SR latch

SRAM cell

# Announcements

## Class session plan

- ▶ Tuesday, 4/23: Diving deeper: Digital logic. (CS:APP Chapter 4.2)  
(Recommended reading: Patterson & Hennessy, Computer organization and design, appendix on "The Basics of Logic Design." Available online via Rutgers Libraries)
- ▶ Thursday, 4/25: Survey of advanced topics in (quantum) computer architecture.
- ▶ Tuesday, 5/7: 12:00-15:00, SERC 111, closed book, closed notes, no electronic devices, no calculator final exam.

# Table of contents

## Announcements

## Functional completeness

The set of logic gates {NOT, AND, OR} is universal

The NAND gate is universal

The NOR gate is universal

## Combinational logic

Decoders

Multiplexers

## PA6 Demo code: directMapped read logic

## Sequential logic


SR latch

SRAM cell

The set of logic gates {NOT, AND, OR} is universal




And

 


$$\text{out} = a \ \&\ \&\ b$$

Or

 

$$\text{out} = a \ || \ b$$

Not

 

$$\text{out} = !a$$

Figure: Source: CS:APP

# The set of logic gates {NOT, AND, OR} is universal


- ▶ Any truth table can be expressed as sum of products form.
- ▶ Write each row with output 1 as a product (minterm).
- ▶ Sum the products (minterm).
- ▶ Forms a disjunctive normal form (DNF).
- ▶  $D = \bar{A}\bar{B}\bar{C} + A\bar{B}C$
- ▶ Always only needs NOT, AND, OR gates.
- ▶ Supplementary slides example...

## Logical Completeness

Can implement ANY truth table with AND, OR, NOT.


A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

Sum of products  
OR of AND clauses

 

1. AND combinations that yield a "1" in the truth table.

2. OR the results of the AND gates.

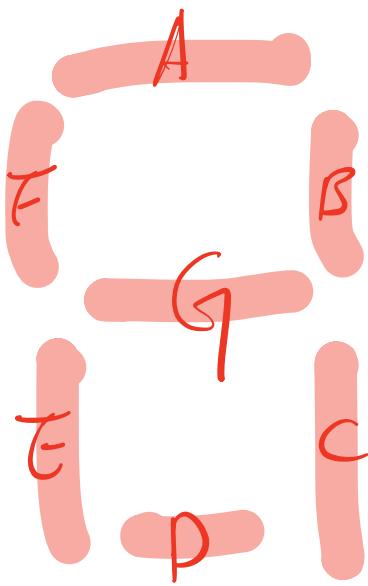

$$E = \{0, 2, 6, 8\}$$

input[3=0]

input[2]

input[1]


input[0]

input[0]

digit	input[3]	[2]	[1]	[0]	E
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	0	1
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	1
7	0	1	1	1	0
8	1	0	0	0	1
9	1	0	0	1	0

$$E = (\bar{3} \cdot \bar{2} \cdot \bar{1} \cdot \bar{0}) + (\bar{2} \cdot \bar{2} \cdot \bar{1} \cdot \bar{0}) + (\bar{2} \cdot \bar{2} \cdot \bar{1} \cdot \bar{0}) + (\bar{2} \cdot \bar{2} \cdot \bar{1} \cdot \bar{0})$$

sum of products, ors - of -ands

 



$\bar{i}_3$

$i_2$

$\bar{i}_1$	$\bar{i}_0$	$\bar{i}_3$	$i_2$
		$\bar{i}_3$	$i_2$
		$\bar{i}_3$	$i_2$
		$\bar{i}_3$	$i_2$
		$\bar{i}_3$	$i_2$
		$\bar{i}_3$	$i_2$
		$\bar{i}_3$	$i_2$
		$\bar{i}_3$	$i_2$

$$F = \bar{i}_1 \bar{i}_0 + \bar{i}_1 i_0 \bar{i}_2$$

$$= \bar{i}_0 (i_1 + \bar{i}_1 \bar{i}_2)$$

# The set of logic gates {NOT, AND, OR} is universal

- ▶ Any truth table can be expressed as sum of products form.
- ▶ Write each row with output 1 as a product (minterm).
- ▶ Sum the products (minterm).
- ▶ Forms a disjunctive normal form (DNF).
- ▶  $D = \bar{A}B\bar{C} + A\bar{B}C$
- ▶ Always only needs NOT, AND, OR gates.
- ▶ Supplementary slides example...


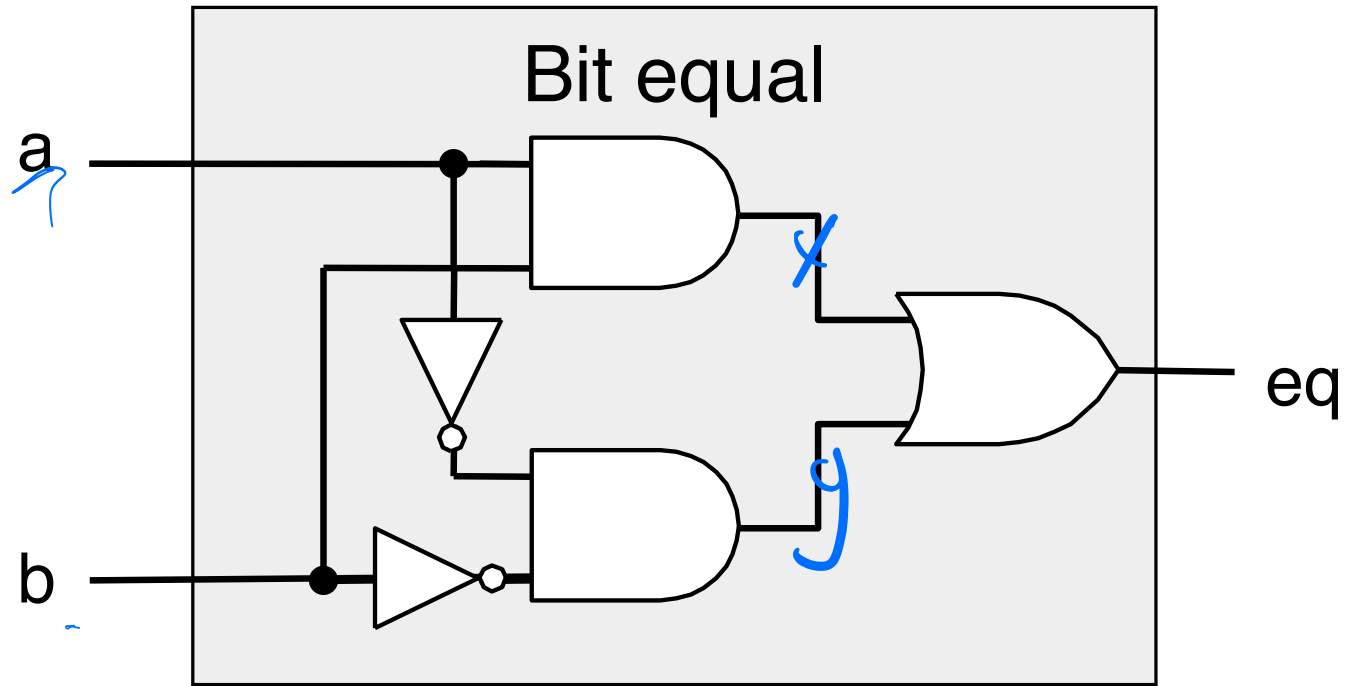


Figure: Source: CS:APP

a	$\bar{a}$	b	$\bar{b}$	x	y	eq
0	1	0	1	0	1	1
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	1


char w char v

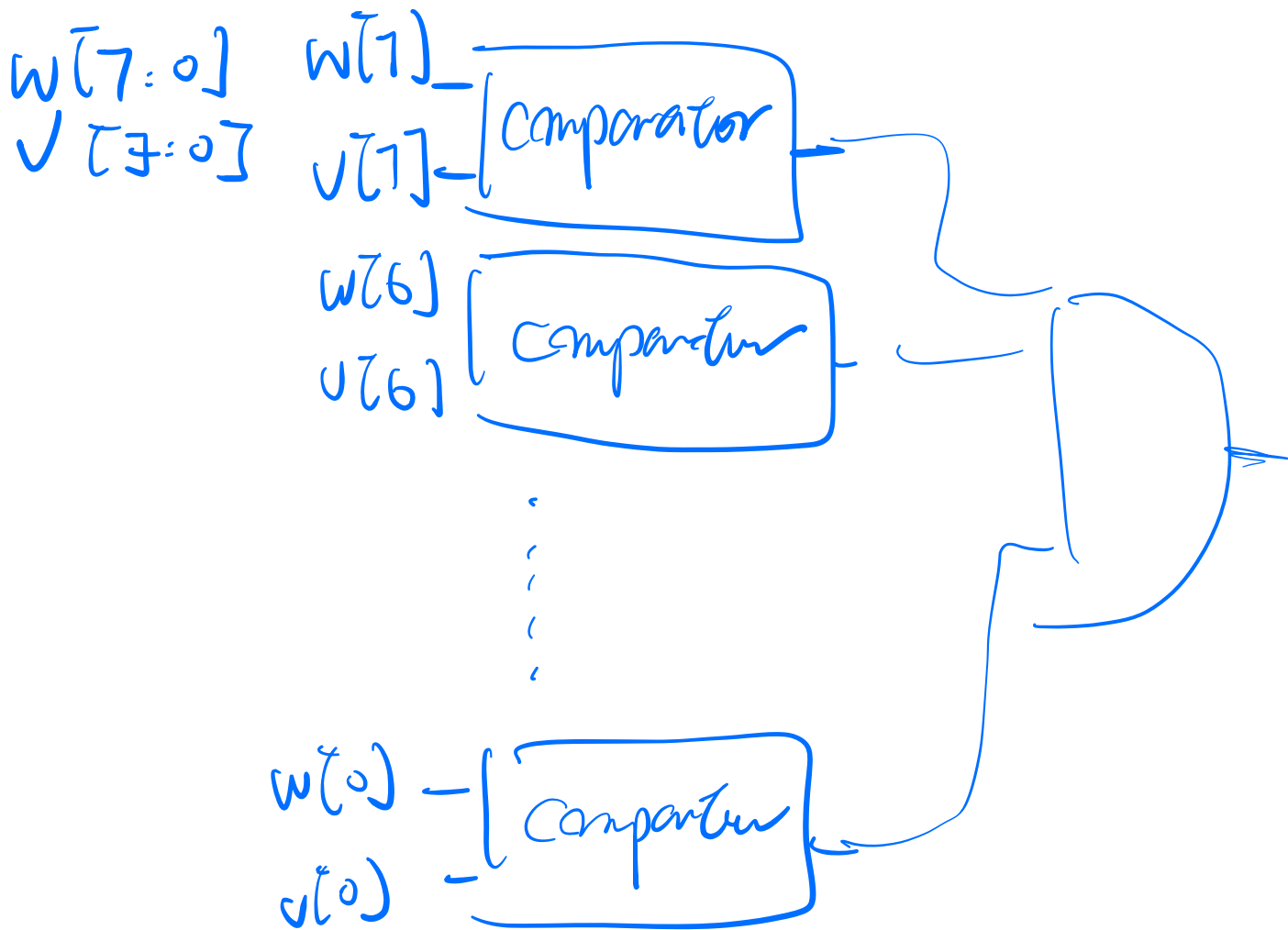

cmpb

# The NAND gate is universal


## NOT gate as a single NAND gate

 

$A$	$\bar{A}$	$AA$	$\overline{AA}$
0	1	0	1
1	0	1	0

Table:  $\bar{A} = \overline{AA}$

## AND gate as two NAND gates

 

$A$	$B$	$AB$	$\overline{AB}$	$\overline{\overline{AB}}$
0	0	0	1	0
0	1	0	1	0
1	0	0	1	0
1	1	1	0	1

Table:  $AB = \overline{\overline{AB}}$



# The NAND gate is universal

## De Morgan's Law

$A$	$B$	$\bar{A}$	$\bar{B}$	$\bar{A}\bar{B}$	$A + B$	$\overline{A + B}$
0	0	1	1	1	0	1
0	1	1	0	0	1	0
1	0	0	1	0	1	0
1	1	0	0	0	1	0


Table:  $\bar{A}\bar{B} = \overline{A + B}$

## OR gate as three NAND gates

  

# The NOR gate is universal


## NOT gate as a single NOR gate

 

A	$\bar{A}$	$A + A$	$\overline{A + A}$
0	1	0	1
1	0	1	0

Table:  $\bar{A} = \overline{A + A}$

## OR gate as two NOR gates

 

A	B	$A + B$	$\overline{A + B}$	$\overline{\overline{A + B}}$
0	0	0	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	0	1

Table:  $A + B = \overline{\overline{A + B}}$



# The NOR gate is universal

## De Morgan's Law

$A$	$B$	$\bar{A}$	$\bar{B}$	$\bar{A} + \bar{B}$	$AB$	$\overline{AB}$
0	0	1	1	1	0	1
0	1	1	0	1	0	1
1	0	0	1	1	0	1
1	1	0	0	0	1	0

Table:  $\bar{A} + \bar{B} = \overline{AB}$

## AND gate as three NOR gates

  

# Combinational vs. sequential logic

## Combinational logic

- ▶ No internal state nor memory
- ▶ Output depends entirely on input
- ▶ Examples: NOT, AND, NAND, OR, NOR, XOR, XNOR gates, decoders, multiplexers.

## Sequential logic

- ▶ Has internal state (memory)
- ▶ Output depends on the inputs and also internal state
- ▶ Examples: latches, flip-flops, Mealy and Moore machines, registers, pipelines, SRAMs.



# Table of contents

## Announcements

## Functional completeness

The set of logic gates {NOT, AND, OR} is universal

The NAND gate is universal

The NOR gate is universal

## Combinational logic

Decoders

Multiplexers

PA6 Demo code: directMapped read logic

## Sequential logic

SR latch

SRAM cell

# Decoders

Takes  $n$ -bit input, uses it as an index to enable exactly one of  $2^n$  outputs

## Internal design of 1:2 decoder

---

 


Figure: Source: Mano & Kime

# Decoders

## Hierarchical design of decoder (2:4 decoder)

Takes  $n$ -bit input, uses it as an index to enable exactly one of  $2^n$  outputs


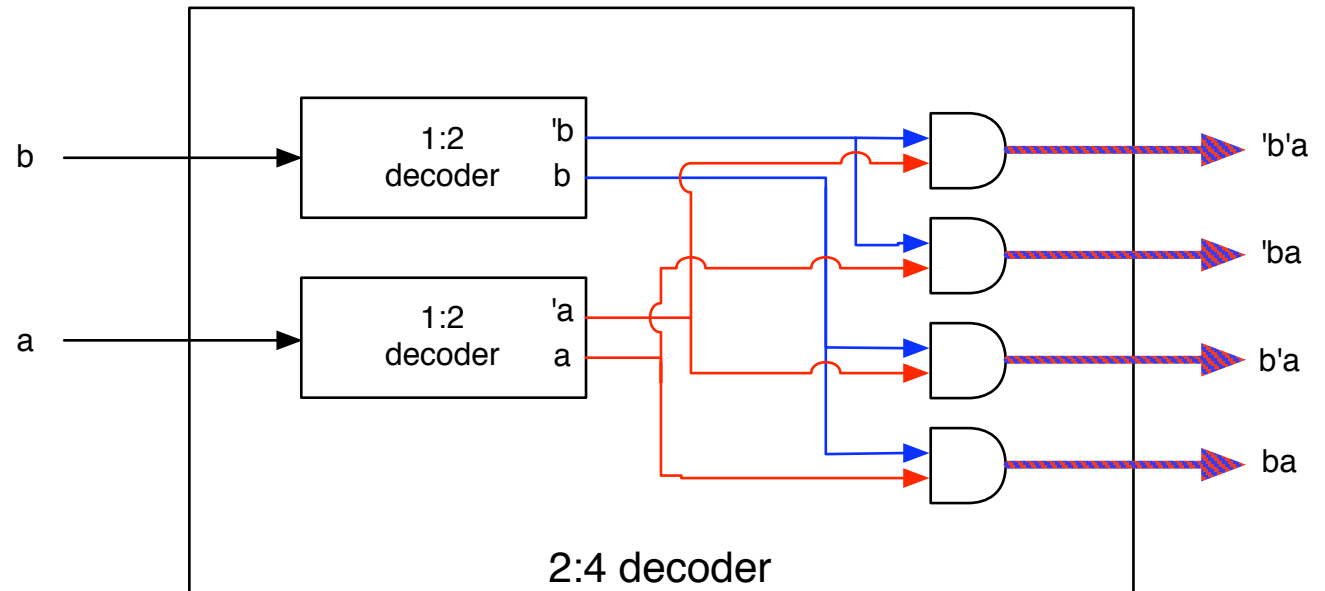


Figure: Source: Mano & Kime

# Decoders
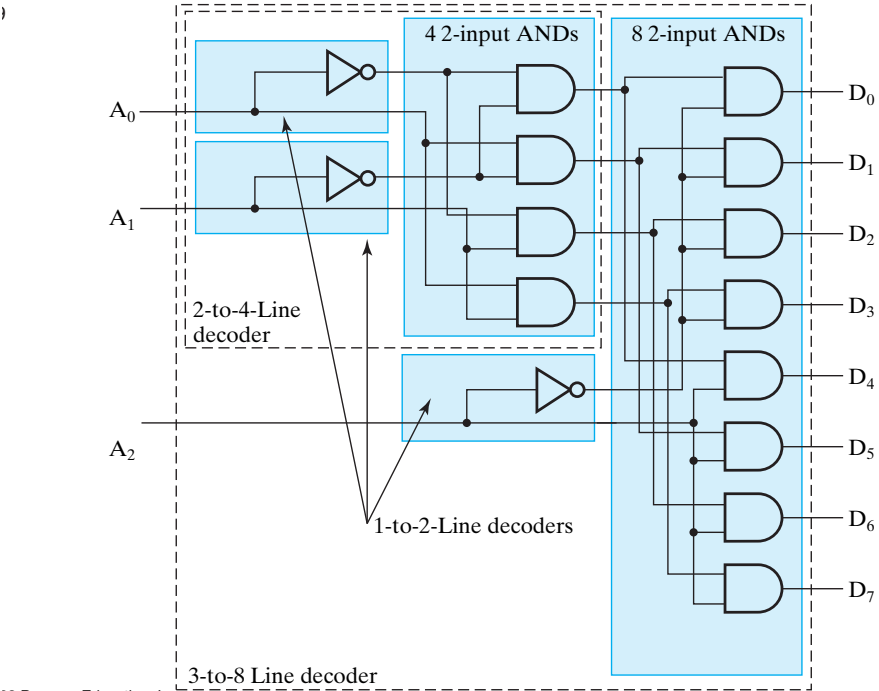
## Decoder (3:8)

Hierarchical design: use small decoders to build bigger decoder



Takes n-bit input, uses it as an index to enable exactly one of  $2^n$  outputs

Note:  $A_2$  “selects” whether the 2-to-4 line decoder is active in the top half ( $A_2=0$ ) or the bottom ( $A_2=1$ )

Figure: Source: Mano & Kime

# Multiplexers

Using n-bit selector input, select among one of  $2^n$  choices

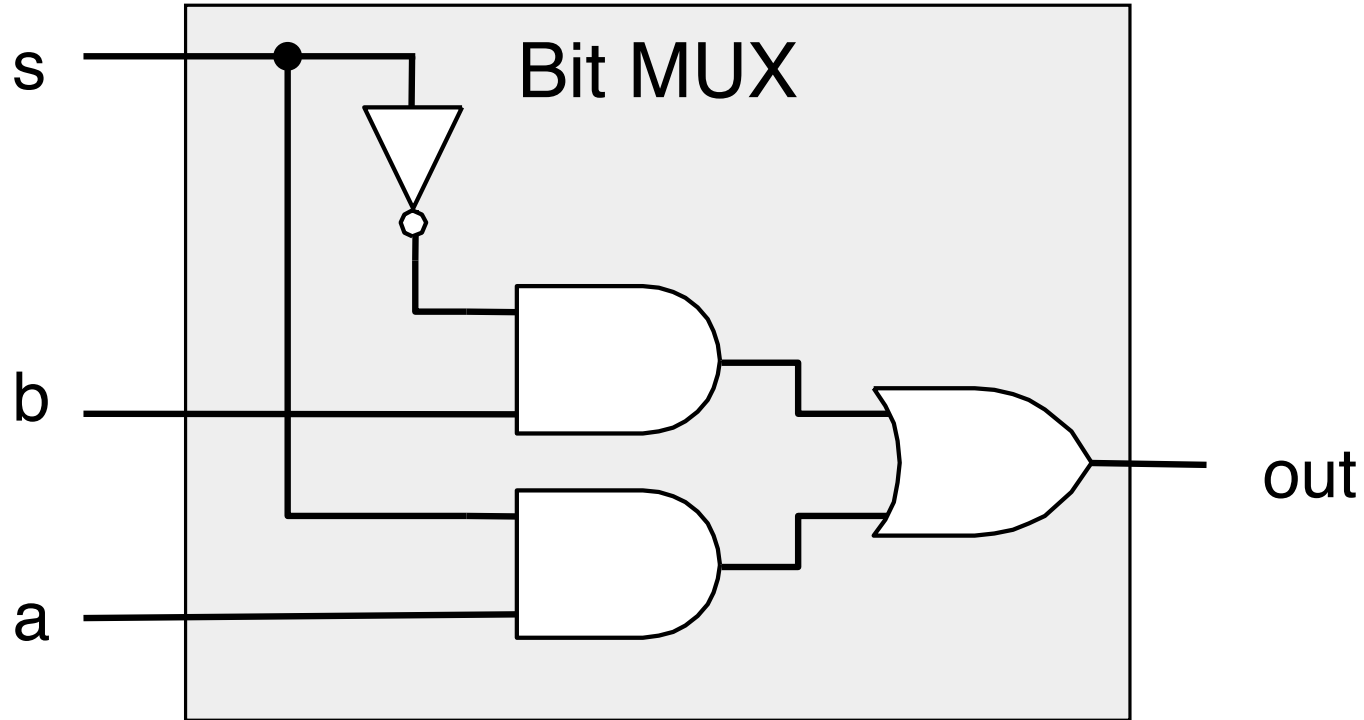


Figure: Source: CS:APP

# Multiplexers

Using n-bit selector input, select among one of  $2^n$  choices

 



Figure: Source: CS:APP

# Multiplexers
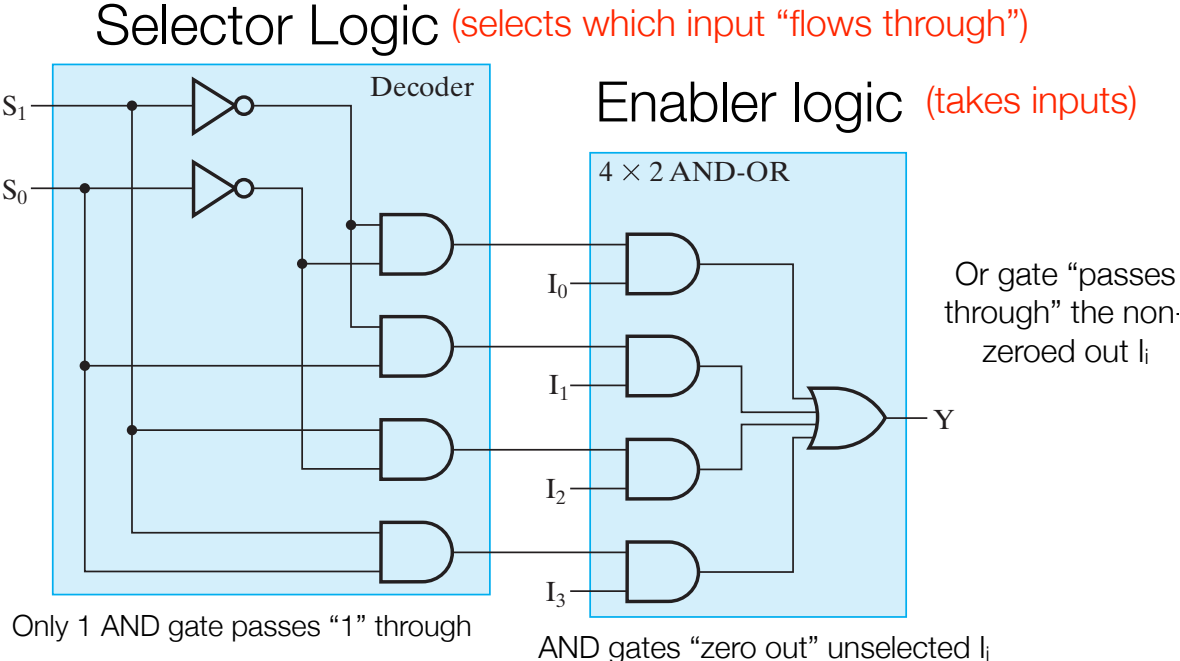
## Internal mux organization

3-26

Using n-bit selector input, select among one of  $2^n$  choices



© 2008 Pearson Education, Inc.  
M. Morris Mano & Charles R. Kime  
LOGIC AND COMPUTER DESIGN FUNDAMENTALS, 4e

Figure: Source: Mano & Kime

# Table of contents

## Announcements

## Functional completeness

The set of logic gates {NOT, AND, OR} is universal

The NAND gate is universal

The NOR gate is universal

## Combinational logic

Decoders

Multiplexers

## PA6 Demo code: directMapped read logic


## Sequential logic

SR latch

SRAM cell



# directMapped read logic

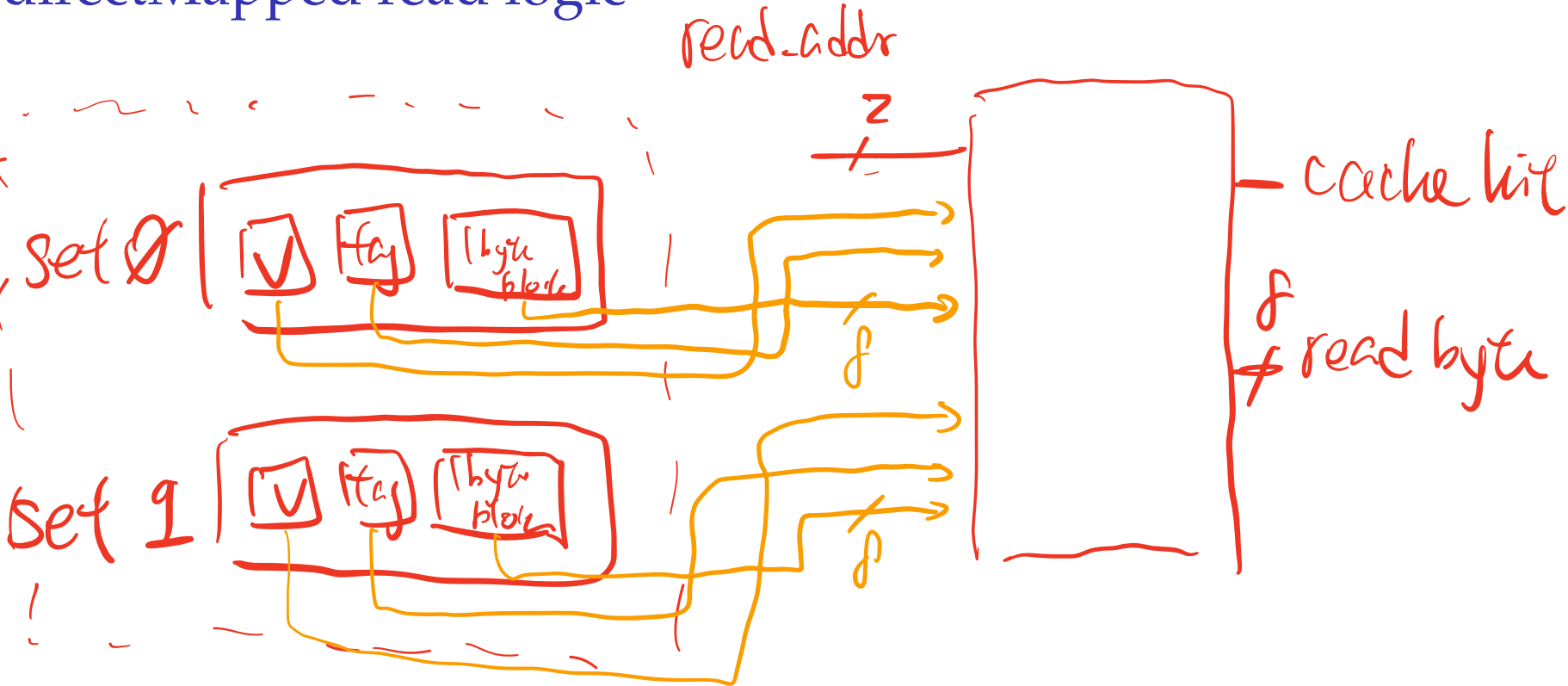

read\_addr [1:0] <sup>2</sup> → read\_addr[0] - set\_index  
read\_addr [2] → tag


set0 valid  
set1 valid → Mux → muxed\_valid

set0 tag  
set1 tag → Mux → muxed\_tag

set0 block  $\delta$   
set1 block  $\delta$  → Mux → muxed\_block

cache hit  
D  
comparator

$\delta$  → read bytes

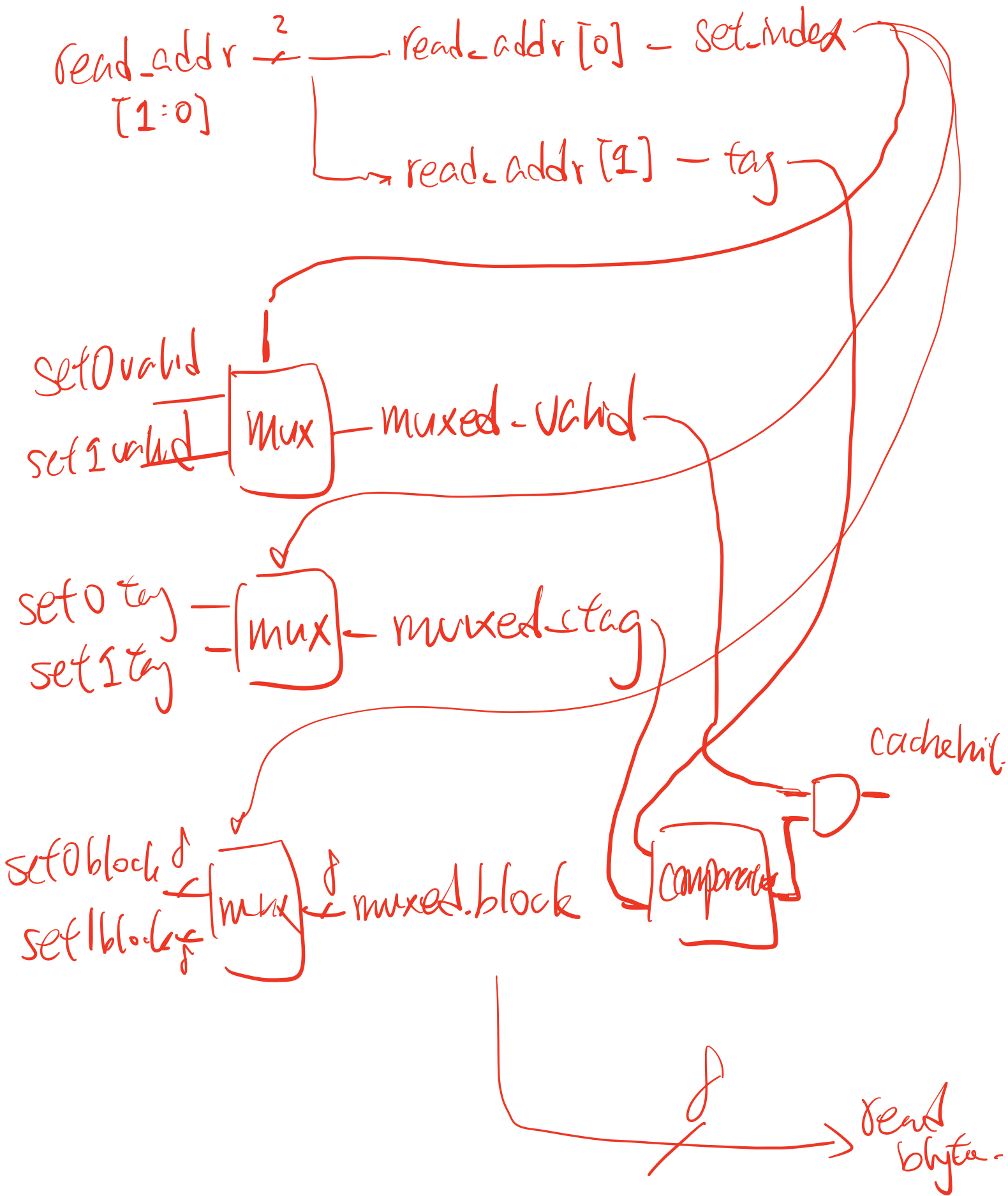

# Table of contents

## Announcements

## Functional completeness

The set of logic gates {NOT, AND, OR} is universal

The NAND gate is universal

The NOR gate is universal

## Combinational logic

Decoders

Multiplexers

## PA6 Demo code: directMapped read logic

## Sequential logic

SR latch

SRAM cell

# Sequential logic

 


Figure: Source: Mano & Kime

# The simplest sequential logic element: The set/reset (SR) latch

## SR latch

- Latch constructed of cross-coupled NOR gates


 


Figure: Source: Mano & Kime
 
# The simplest sequential logic element: The set/reset (SR) latch



R	S	Q	$\overline{Q}$
0	0	Q	$\overline{Q}$
0	1	1	0
1	0	0	1
1	1		

Hold previous value

Figure: Source: Mano & Kime

# 6 transistor SRAM cell


 


Figure: Source: Wikimedia


# Asynchronous / Synchronous circuits

Timing

Circuit:

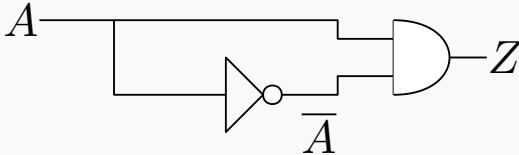

Voltages over time:

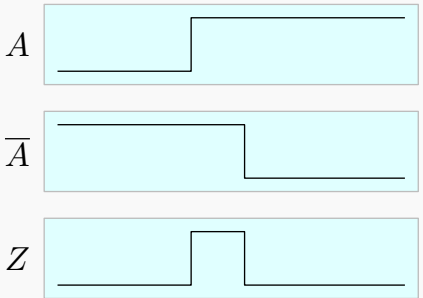

13